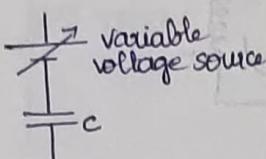


\rightarrow stores voltage in the form of electric charge
 \rightarrow stores current in the form of magnetic field.


$$C \frac{1}{T} \leftrightarrow \text{equivalent to}$$



When no charge is stored in C, voltage source is at 0V.

$$L = 5H$$


$$\leftrightarrow \text{equivalent to}$$

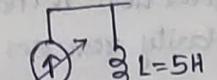

When inductor is not excited, current source gives 0A


Voltage source: Voltage does not change even when it is open-circuited
Current source: Current does not change even when it is short-circuited

Time Constant

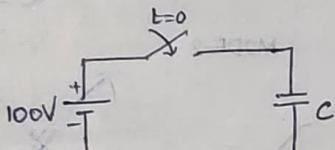

$$\text{At } t=0, V_c = 100V$$

x

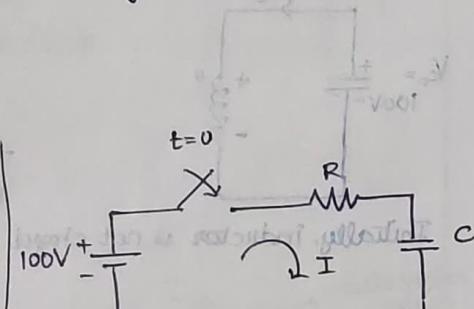


$$\text{At } t=0, V_c = (100 - IR) \text{ Volts}$$

$$\text{At } t=\infty, V_c = 100V$$


x

Charging

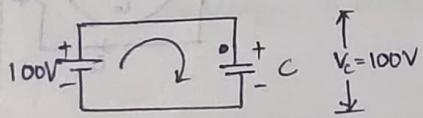

during charging, current enters through + side

Discharging

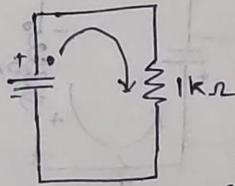


during discharging current leaves through + side


In capacitors,
 during charging & discharging \Rightarrow current polarity changes
 \Rightarrow voltage polarity remains same

Inductors

Charging

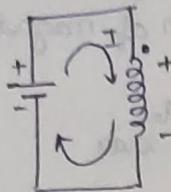

Discharging

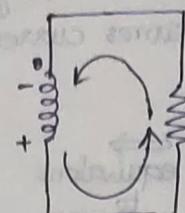

In inductors, during charging & discharging,


→ current direction remains same

→ voltage polarity reverses.

Tank-LCR (assuming no loss)

Initially, cap is charged at

100V

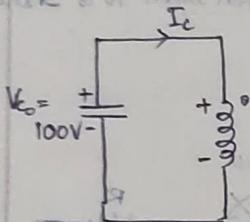


Initially, inductor is not charged.

Mode-1


When capacitor is completely discharged, $V_c = 0$, the inductor current is at max. position.

Mode-2

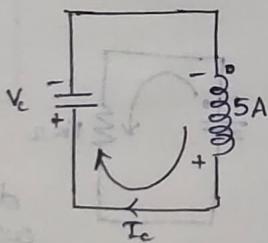


Inductor will charge the capacitor in reverse direction.

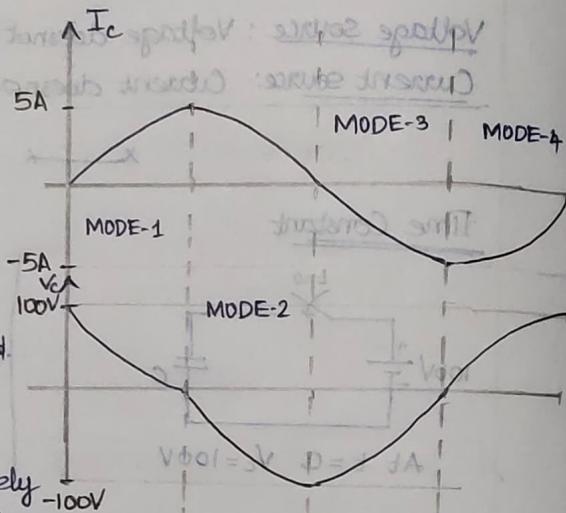
Once cap. voltage reaches 100V
I_c will be zero



Mode-3

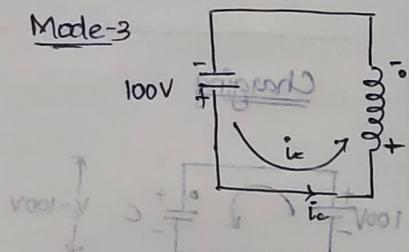

Mode-4

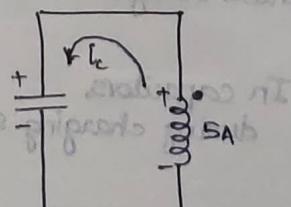

* Nowadays, in ICs Silicon wafer is not used

* Transistors ⇒ Building blocks of ICs

AUG
9 2021POWER DEVICES

- (i) Power diodes
- (ii) Power BJT
- (iii) IGBT ✓
- (iv) MOSFET ✓


(v) SCR ✓

(vi) DIAC

(vii) TRIAC


VI Characteristics
Working Principle
Diagram

does not come under PE

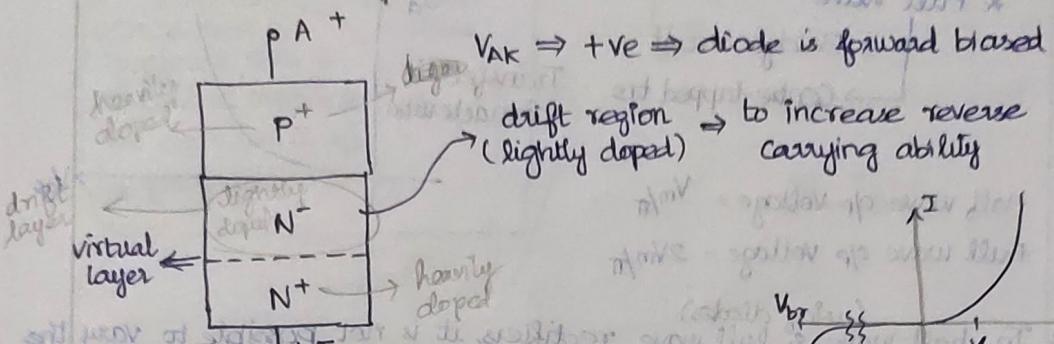POWER DIODE

Working principle → same as normal diode

$$V_f = 0.6 \text{ for Si} \\ = 0.3 \text{ for Ge}$$

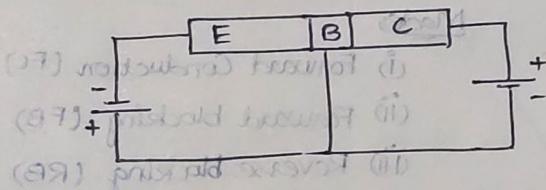Width of N- region
(lightly doped region)POWER BJT

* acts as switch in saturation & cut-off region
 " amplifier in linear region


IGBT (IGIBJT)

→ Insulated Gate BJT

takes very less current to turn on

(Advantage)

Power consumption is less

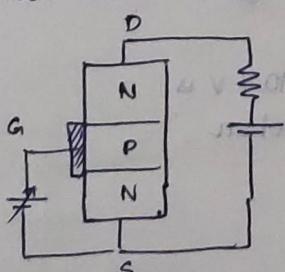MOSFET - Metal Oxide semi-conductor Field effect Transistor

- * enhancement type MOSFET
- * depletion type MOSFET

SCR - Silicon Controlled Rectifier

Rectifiers already studied.

* Half Wave

* Full Wave

↳ Bridge circuit

↳ Centre-tapped trs



Half wave outputs

Full wave outputs


$$\text{Half wave o/p voltage} = V_m/\pi$$

$$\text{Full wave o/p voltage} = 2V_m/\pi$$

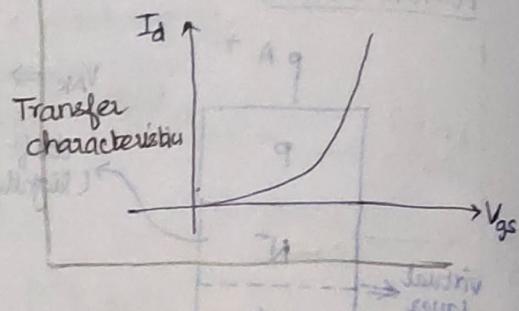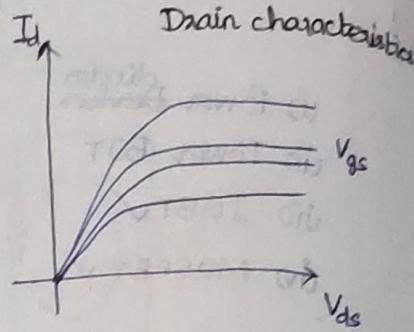- * In half wave & full wave rectifiers, it is not possible to vary the output voltage without changing the i/p voltage \Rightarrow uncontrolled rectifiers



SCR

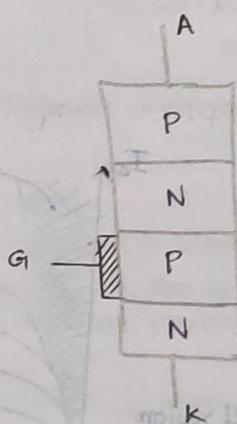

* three terminal device
(A-Anode, K-Cathode, G-Gate)

Working Principles

Modes

- Forward Conduction (FC)
- Forward blocking (FB)
- Reverse blocking (RB)

Mode-1 (FC Mode)

$V_{AK} \Rightarrow +ve$ (forward bias)



A \Rightarrow +ve Volt K \Rightarrow -ve Volt

\Rightarrow J1 & J3 junctions are forward biased

\Rightarrow So all voltage will appear across the junction J2

\Rightarrow To make the J2 region conduct, we have to give atleast 10.7V to make it forward biased for a very short time.

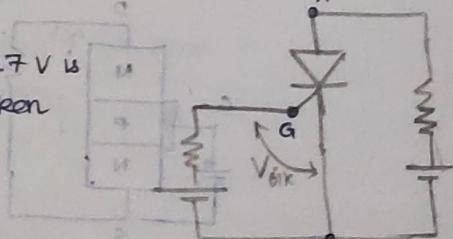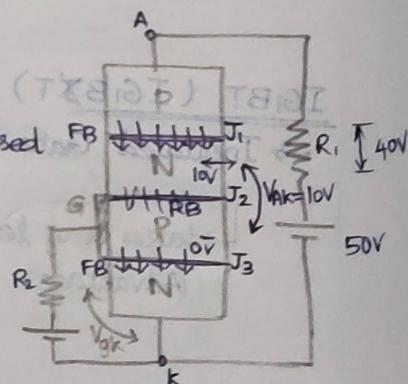
\Rightarrow For a very short time, if 10.7V is given, J2 junction will be broken and SCR starts conducting.



* We can't stop the conduction by removing the gate voltage.

Aug 11
2021

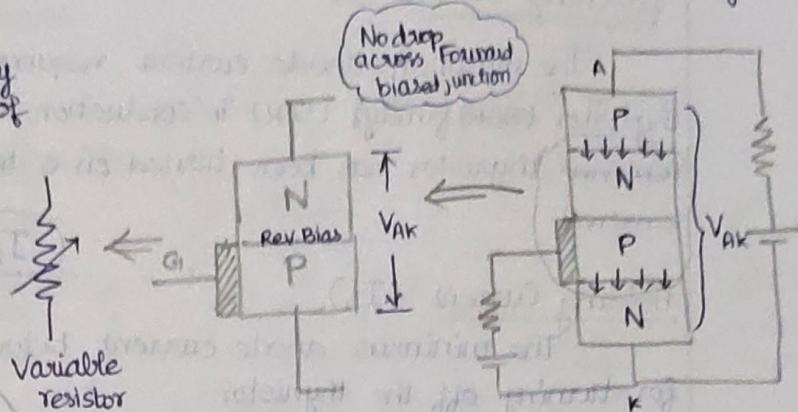
In rev. bias, very small amount of leakage current flows.



* Once SCR is triggered, there is no control over SCR. We can't turn it off by giving gate voltage.

state n3
path switch
closed

At $I_g = 0$

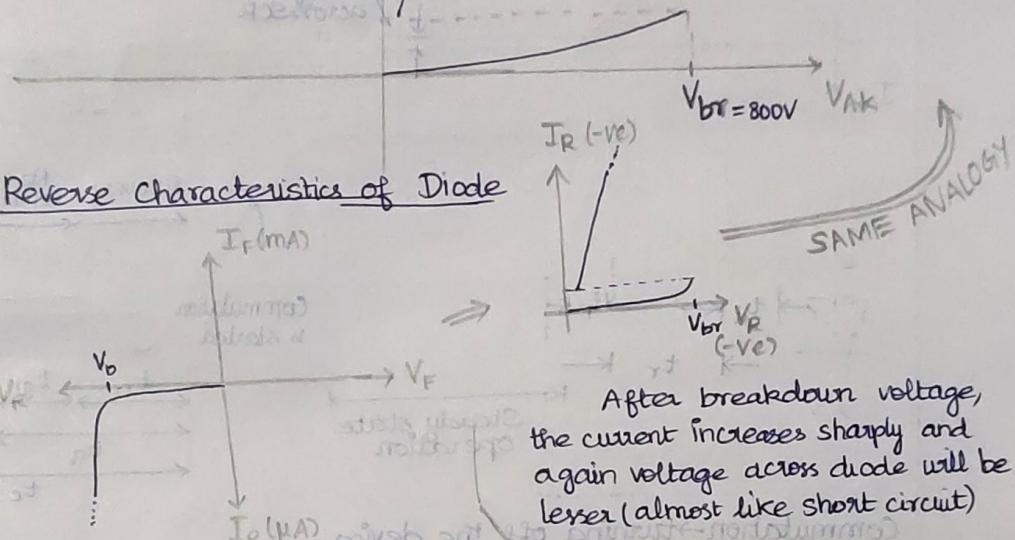


After breakdown voltage, the current increases sharply and again voltage across diode will be lesser (almost like short circuit)

* After the -ve voltage of diode is increased further beyond breakdown voltage, current increases sharply (as irreversible damage of diode occurred)

* Before -ve voltage reaching V_b , current is in micro amperes.

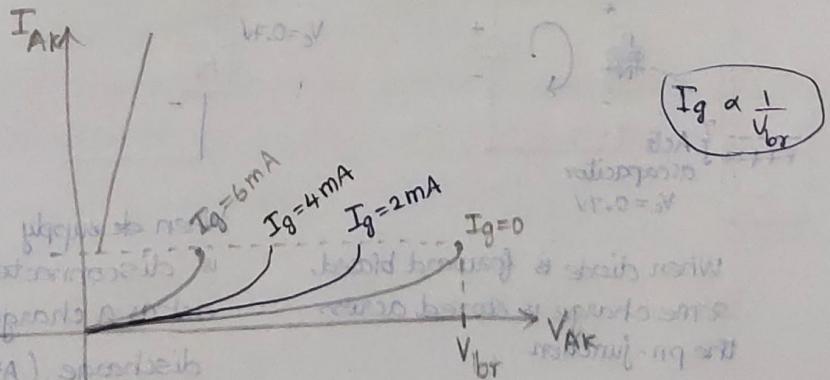When I_g is increased, the junction J2 is slightly forward biased ($I_g = 2 \text{ mA}$) \Rightarrow so lesser voltage across Ak (V_{Ak}) is required to turn on the reverse bias region.




Latching Current (I_L)

The minimum anode current required to maintain the thyristor (SCR) family in conduction, immediately after removing thyristor has been turned on & the gate signal is removed.

$$I_L > I_h$$

Holding Current (I_h)

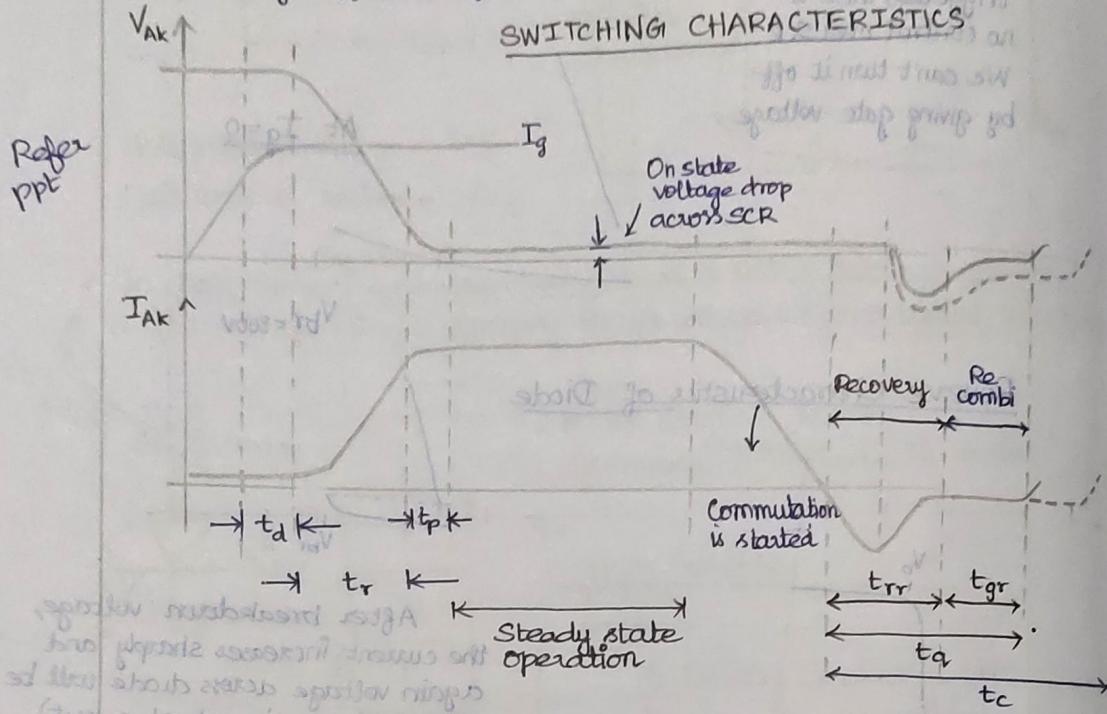The minimum anode current below which it must fall for turning off the thyristor.




Commutation \rightarrow turning off the device

- where t_d - delay time; t_r - rise time; t_p - peak time; t_{rr} - reverse recovery time; t_{gr} - gate recovery time; t_q - turn off time; t_c - ckt commutation time

Explanation for why t_{rr} , i is negative?

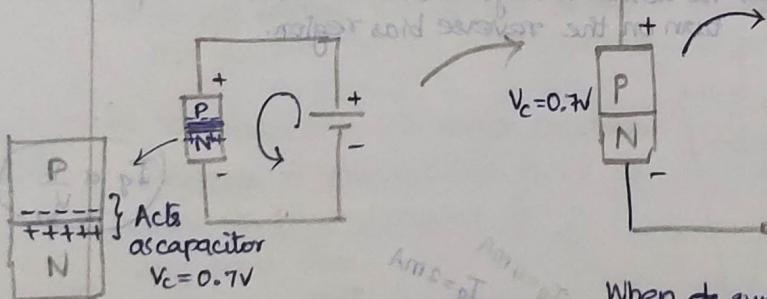
Consider, if there is no reverse current, then $i = 0$ and $V_c = 0$. As a result, $A_m = 0$ and $i = 0$.



When diode is forward biased, some charge is stored across the pn-junction


When dc supply is disconnected, the diode will act as a charged capacitor and discharge. (At this time, current flows in opposite direction)

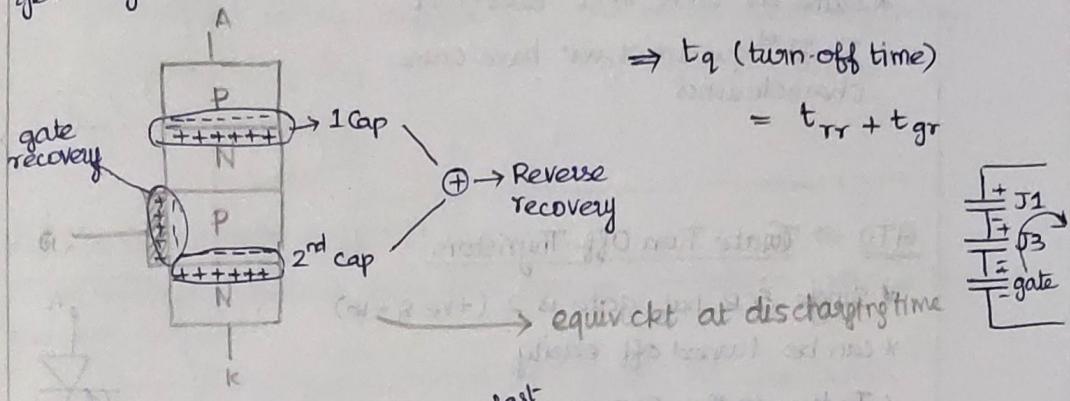Due to this discharging phenomena, at commutation time, we get negative current.



To make this discharging process fast, high resistance is added so as the time constant increases

$$\text{Discharging time} = \text{Time Constant} = RC$$

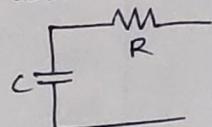

Aug 13
2021


TURN OFF TIME

Initially, diode is forward biased, to turn off the diode, we need to give reverse bias for atleast $1 t_{tr}$

Turn-off time

minimum time required to turn off the SCR

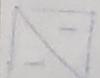Commutation time: minimum time required to turn off SCR with external circuit.




SCR commutation of transient supports
a current & allows


TRIAC

* two SCRs connected in anti-parallel fashion

Symbol

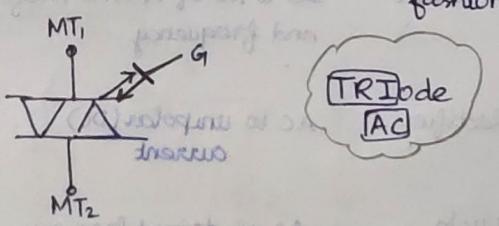

Equivalent circuit of TRIAC

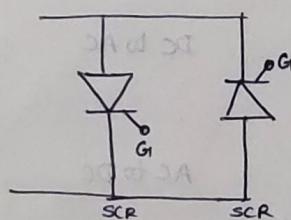


* Terminals can be interchangable.

* For AC supply given, any one SCR will conduct for +ve half cycle and another will conduct for -ve half cycle

* Gate voltage given to G1 terminal will be applied to the SCR that is conducting.

Applications:- AC Voltage controllers

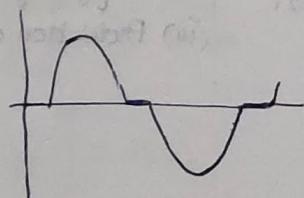



Characteristics of Triac

- * Same as SCR in Ist Quadrant
- * In IIIrd quadrant, we have same characteristics

GTO \Rightarrow Gate Turn Off Thyristors

- * Single SCR but gate is 2 (+ve & -ve)
- * can be turned off easily

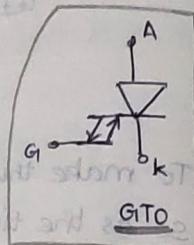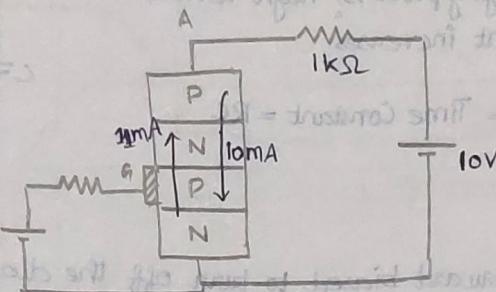* To turn on the SCR, +ve gate pulse is given



- * To turn off the SCR, -ve gate pulse of 11mA is given. It is turn off the SCR.

POWER CONVERTER TOPOLOGIES

Conversion	Name	Function	Symbol
DC to DC	Chopper	Constant to variable DC or Variable to constant DC	
DC to AC	Inverter	DC to AC of desired voltage and frequency	
AC to DC	Rectifier	AC to unipolar (DC) current	
AC to AC	Cyclo converter, AC-PAC, Matrix converter	AC of desired frequency and/or magnitude from generally line AC	

Aug 18
2021

- Triggering methods
- Protection of SCR
- Commutation of SCR

TRIGGERING METHODS

(a) Forward voltage triggering

(b) Gate triggering

(c) $\frac{dV}{dt}$ triggering

(d) Temperature triggering

(e) Light triggering

(a) Forward voltage triggering:

* Applying voltage more than reverse breakdown voltage to make the SCR conduct.


* Irreversible damage occurs. SCR cannot be used again.

(b) Gate triggering:

* By applying gate voltage, the SCR is made to conduct. (seen earlier)

* Three types

① R triggering ② RC trig ③ UJT trig

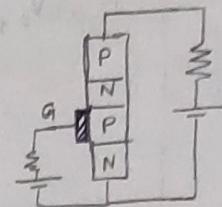

Commutation

N = Natural commutation (uses $\frac{1}{2} \pi$)

Forced commutation


* voltage commutation * load commutation (self commutation)

* current or resonant pulse * external pulse



HALF & FULL WAVE (UNCONTROLLED RECTIFIERS)

31/08/2021

Uncontrolled Rectifiers

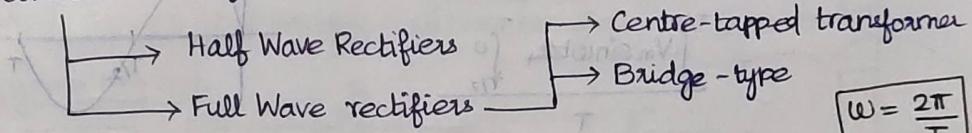

Half-Wave rectifiers

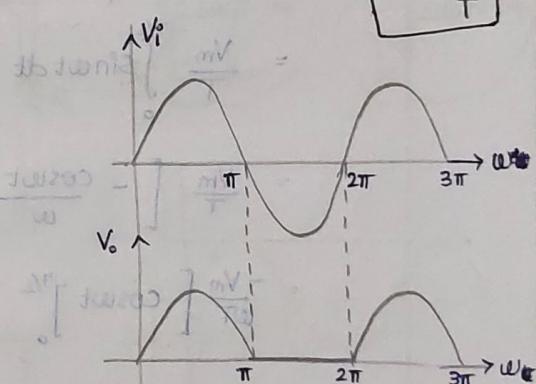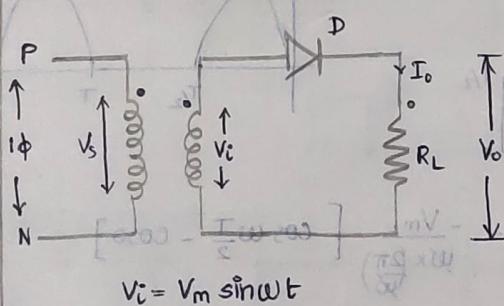

$$[\text{In method }] \frac{mV}{\pi} = [0.203 - \frac{\pi}{2} \times \frac{mV}{\pi}] \frac{mV}{\pi}$$

$$V_{o \text{ avg}} = \frac{\text{Area under the curve for one time period}}{\text{One time period}} = \frac{\text{Area}}{\text{Base}}$$

$$\frac{mV}{\pi} = ((\text{--})) \frac{mV}{\pi} \cdot \frac{mV}{\pi}$$

$$= \frac{\int_0^{2\pi} V_o d\omega}{2\pi} = \frac{\int_0^{\pi} V_m \sin(\omega t) d(\omega t) + \int_{\pi}^{2\pi} 0 d(\omega t)}{2\pi}$$

$$\begin{aligned}
 V_o \text{ avg} &= \frac{1}{2\pi} \int_0^\pi V_m \sin(\omega t) dt \\
 &= \frac{V_m}{2\pi} \left[-\frac{\cos(\omega t)}{\omega} \right]_0^\pi \\
 &= \frac{-V_m}{2\pi} [+\cos\pi - \cos 0] = \frac{-V_m}{2\pi} [+(-1) - 1]
 \end{aligned}$$

$\boxed{V_o \text{ avg} = \frac{V_m}{\pi}}$ Half wave rectifier


method $V_o \text{ rms} = \sqrt{\frac{(\text{Area under the curve})^2}{\text{Base}}}$

$$\begin{aligned}
 &= \sqrt{\frac{\int_0^\pi V_m^2 \sin^2(\omega t) dt}{2\pi}} = \sqrt{\frac{V_m^2}{2\pi} \int_0^\pi \sin^2 \omega t dt} \\
 &= \sqrt{\frac{V_m^2}{2\pi} \int_0^\pi \left(\frac{1}{2} - \frac{\cos 2\omega t}{2} \right) dt} = \frac{V_m}{2} \quad \boxed{V_o \text{ rms} = \frac{V_m}{2}}
 \end{aligned}$$


Half wave rectifier

Average voltage of HWR (Uncontrolled)
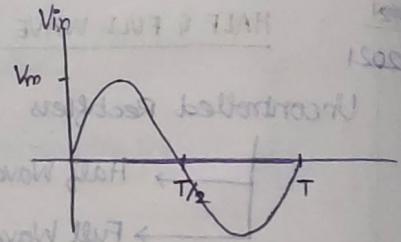
$$V_o \text{ avg} = \frac{\text{Area}}{\text{Base}} = \frac{\int_0^T V_o}{T}$$


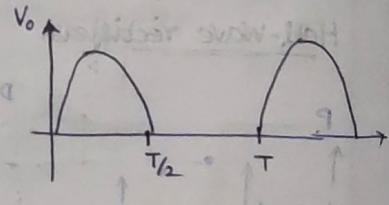
$$= \frac{V_m}{T} \int_0^{T/2} \sin \omega t dt$$



$$= \frac{V_m}{T} \left[-\frac{\cos \omega t}{\omega} \right]_0^{T/2}$$

$$= -\frac{V_m}{\omega T} \left[\cos \omega t \right]_0^{T/2} = -\frac{V_m}{\omega \times \frac{2\pi}{\omega}} \left[\cos \frac{\omega T}{2} - \cos 0 \right]$$

$$= -\frac{V_m}{2\pi} \left[\cos \frac{2\pi \times \frac{T}{2}}{\omega} - \cos 0 \right] = -\frac{V_m}{2\pi} [\cos \pi - \cos 0]$$

$$= -\frac{V_m}{2\pi} [-1 - 1] = -\frac{V_m}{2\pi} (-(-2)) = \frac{V_m}{\pi} \checkmark$$

$$\frac{w_b}{R_L} \left(1 + \frac{w_b(R_L)}{w_b n V} \right) = \frac{w_b V}{R_L}$$

RMS Voltage of HWR output voltage:


$$\begin{aligned}
 V_{o\text{ rms}} &= \sqrt{\frac{1}{T} \left(\int_0^{T/2} V_m^2 \sin^2 \omega t dt + \int_{T/2}^T V_m^2 \sin^2 \omega t dt \right)} \\
 &= \sqrt{\frac{1}{T} \int_0^{T/2} V_m^2 \sin^2 \omega t dt} = \sqrt{\frac{V_m^2}{T} \int_0^{T/2} \sin^2 \omega t dt} \\
 &= \sqrt{\frac{V_m^2}{T} \int_0^{T/2} \frac{1 - \cos 2\omega t}{2} dt} = \sqrt{\frac{V_m^2}{2T} \int_0^{T/2} (1 - \cos 2\omega t) dt} \\
 &= \sqrt{\frac{V_m^2}{2T} \left[t - \frac{\sin 2\omega t}{2\omega} \right]_0^{T/2}} = \sqrt{\frac{V_m^2}{2T} \left[\left(\frac{T}{2}\right) \frac{\sin 2\omega T}{2\omega} \right] - [0-0]} \\
 &= \sqrt{\frac{V_m^2}{2T} \left[\frac{T}{2} - \frac{\sin \omega T}{\omega} \right]} = \sqrt{\frac{V_m^2}{2T} \left[\frac{T}{2} - \frac{\sin(2\pi \times T)}{2 \times 2\pi} \right]} \\
 &= \sqrt{\frac{V_m^2}{2T} \left[\frac{T}{2} - 0 \right]} = \sqrt{\frac{V_m^2 \times T}{4\pi}}
 \end{aligned}$$

$\sin 2\pi = 0$


$$V_{o\text{ rms}} = \frac{V_m}{2}$$

(Uncontrolled)
CENTER TAPPED TRANSFORMER - Full Wave Rectifier



during (+)ve half cycle

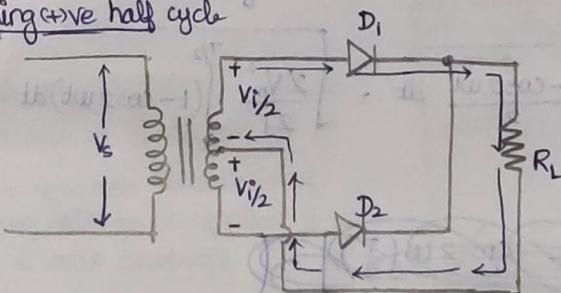

same analogy

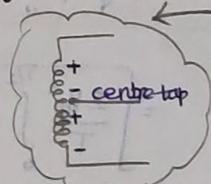

during (-)ve half cycle

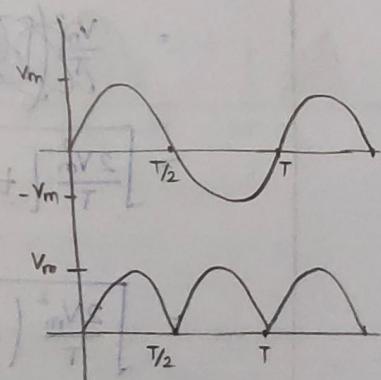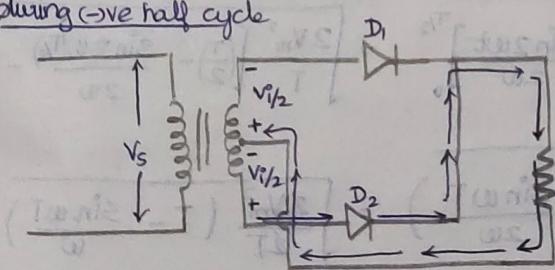

$$\begin{aligned}
 \frac{T}{2} \text{ mV} + (0-T) \times \frac{5\text{ mV}}{T} &= \left(\frac{-5\text{ mV}}{\frac{T}{2}} - T \right) \frac{5\text{ mV}}{T} =
 \end{aligned}$$

V_o avg



V_o avg - Area under one base

Base

$$= \frac{\int_0^{T/2} V_m \sin \omega t dt}{\left(\frac{T}{2}\right)} = \frac{2V_m}{T} \int_0^{T/2} \sin \omega t dt$$

$$= \frac{2V_m}{T} \left[-\frac{\cos \omega t}{\omega} \right]_0^{T/2} = \frac{-2V_m}{\omega T} \left[\cos \omega t \right]_0^{T/2}$$

Base = Time Period
for which V_o repeats

$$\left[\frac{-2V_m}{(2\pi)\omega T} \left[\cos \omega \frac{T}{2} - \cos 0 \right] \right] = \frac{-2V_m}{2\pi} \left[\cos \frac{2\pi}{T} \times \frac{T}{2} - \cos 0 \right]$$

$$V_o \text{ avg} = \frac{2V_m}{\pi}$$

Full Wave

Uncontrolled rectifier

$$V_o \text{ rms} = \sqrt{\frac{1}{\left(\frac{T}{2}\right)} \int_0^{T/2} (V_m \sin \omega t)^2 dt}$$

$$V_{rms} = \sqrt{\frac{1}{T_0} \int_0^T V(t)^2 dt}$$

$$= \sqrt{\frac{2}{T} \int_0^{T/2} V_m^2 \sin^2 \omega t dt} = \sqrt{\frac{2V_m^2}{T} \int_0^{T/2} \sin^2 \omega t dt}$$

$$= \sqrt{\frac{2V_m^2}{T} \int_0^{T/2} \frac{1 - \cos 2\omega t}{2} dt} = \sqrt{\frac{2V_m^2}{2T} \int_0^{T/2} (1 - \cos 2\omega t) dt}$$

$$= \sqrt{\frac{2V_m^2}{T} \left[t - \frac{\sin 2\omega t}{2\omega} \right]_0^{T/2}}$$

$$= \sqrt{\frac{2V_m^2}{T} \left[\left(\frac{T}{2}\right) - \frac{\sin 2\omega (T/2)}{2\omega} - (0-0) \right]}$$

$$= \sqrt{\frac{2V_m^2}{T} \left(\frac{T}{2} - \frac{\sin \omega T}{\omega} \right)}$$

$$= \sqrt{\frac{V_m^2}{T} \left(T - \frac{\sin \frac{2\pi}{T} \times T}{\frac{2\pi}{T}} \right)} = \sqrt{\frac{V_m^2}{T} \times (T - 0)} = \sqrt{\frac{V_m^2 \times T}{T}}$$

$$= \frac{V_m}{\sqrt{2}}$$

03-07-2021

CONTROLLED RECTIFIERS (Converters)

Half-Wave rectifier


Full-wave rectifiers

Center-tapped transist type

Bridge type

Half-controlled
(aka semi-controlled)
converterFully controlled
(full converter)

* Half-controlled is a full wave rectifier.

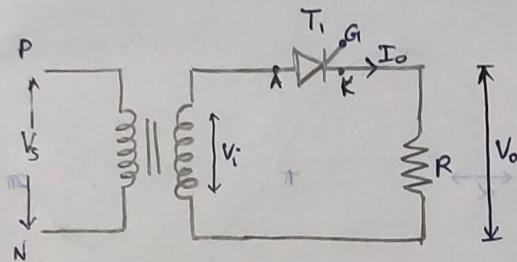HALF WAVE CONTROLLED RECTIFIER (R-load) T_1 - Thyristor-1


$$V_i = V_m \sin \omega t$$

- * In 0 to π , SCR will conduct if SCR is triggered by gate pulse
- * At α time period, gate pulse is applied

- * At π to 2π , SCR is reverse biased $\Rightarrow V_o = 0V$

In reverse bias, even if gate voltage is applied, $V_o = 0V$
(SCR won't conduct)

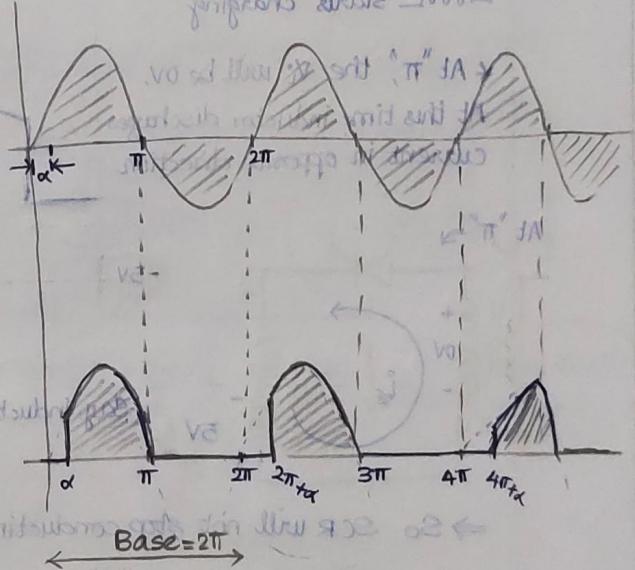- * After $(2\pi + \alpha)$, gate pulse is given, SCR turns on



$$V_{o \text{ avg}} = \frac{\text{Area}}{\text{Base}}$$

$$= \frac{1}{2\pi} \int_{0}^{2\pi} V_o(\omega t) d(\omega t)$$

$$= \frac{1}{2\pi} \left\{ \int_0^\alpha + \int_{V_m \sin \omega t}^{V_m} \int_0^{\omega t} d(\omega t) + \int_\alpha^{2\pi} \right\}$$


$$\frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \cdot d(\omega t) = \frac{V_m}{2\pi} \left[-\frac{\cos \omega t}{1} \right]_{\alpha}^{\pi}$$

$$= -\frac{V_m}{2\pi} [\cos(\pi) - \cos\alpha] = \frac{-V_m}{2\pi} [(-1) - \cos\alpha]$$

$$V_o \text{ avg} = \frac{V_m}{2\pi} (1 + \cos\alpha)$$

HW controlled rectifier
(for R-load)

Half-wave controlled Rectifier (RL load)

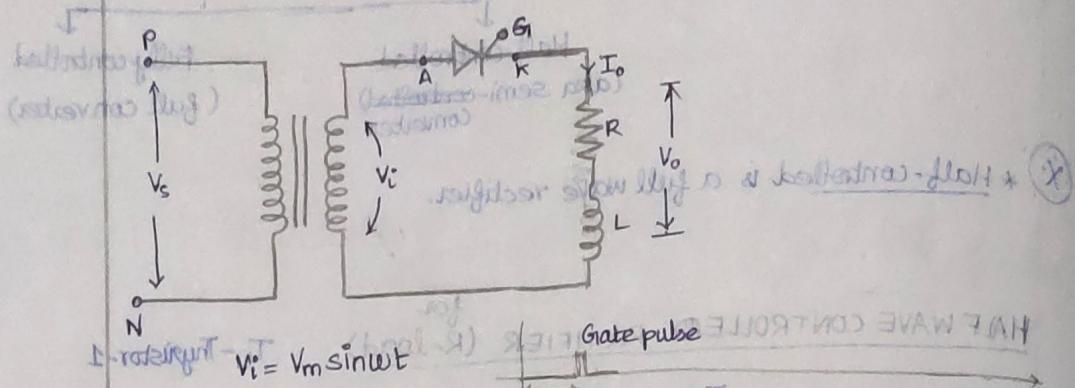



- * At a time period, gate pulse is applied.

In +ve half cycle, SCR is on and it conducts

- * After SCR starts conducting, inductor starts charging

- * At " π ", the V_i will be 0V.

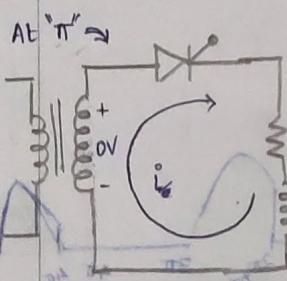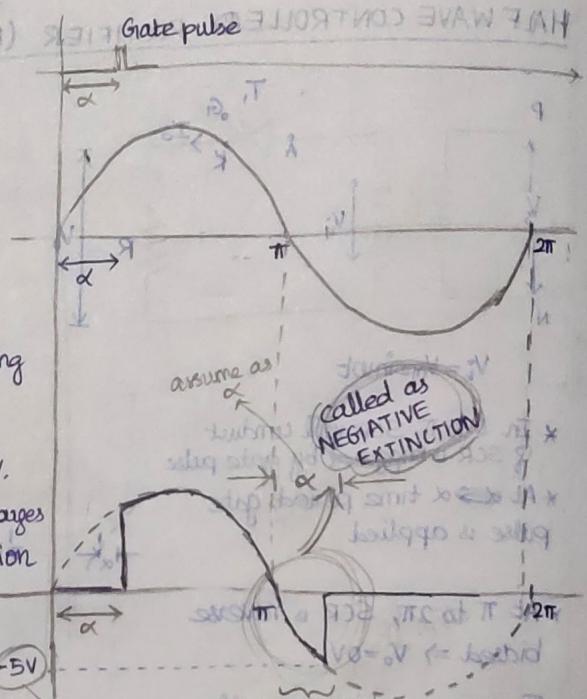At this time inductor discharges current in opposite direction




⇒ So SCR will not stop conducting. It will continuously conduct.

- * After sometime after " π ", the V_i will also reverse its direction (in -ve half cycle)

- * When V_i is exactly -5V AC, no current flows so SCR will turn off.


- * Assume negative extinction time as α for easier calculation
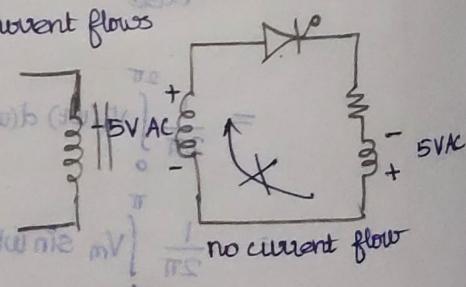
$$\left[\frac{\omega \cos \alpha}{1} - \right] \frac{mV}{T_S} = (\omega b) \cdot \text{dutne mV}$$



$$V_o \text{ avg} = \frac{\text{Area}}{\text{Base}} = \frac{\text{Area}}{2\pi}$$
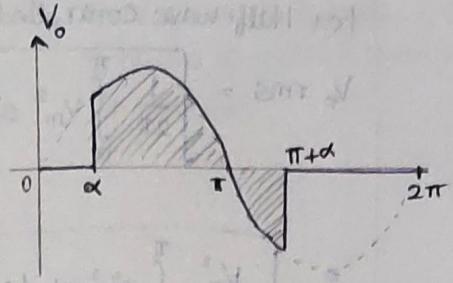
$$= \frac{1}{2\pi} \left\{ \int_0^\alpha 0 + \int_\alpha^{\pi+\alpha} V_m \sin \omega t d(\omega t) + \int_{\pi+\alpha}^{2\pi} 0 \right\}$$



$$= \frac{1}{2\pi} \left\{ V_m \int_\alpha^{\pi+\alpha} \sin \omega t d(\omega t) \right\} = \frac{V_m}{2\pi} \left[-\frac{\cos \omega t}{1} \right]_\alpha^{\pi+\alpha}$$

$$= \frac{-V_m}{2\pi} \left[\cos \omega t \right]_\alpha^{\pi+\alpha} = -\frac{V_m}{2\pi} [\cos(\pi+\alpha) - \cos(\alpha)]$$

$$V_o \text{ avg} = \frac{V_m}{\pi} \cos \alpha$$

$$V_o \text{ rms} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} (V_o(\omega t))^2 d(\omega t)}$$

$$V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T v(t)^2 dt}$$

$$= \sqrt{\frac{1}{2\pi} \int_\alpha^{\pi+\alpha} V_m^2 \sin^2(\omega t) d(\omega t)} = \sqrt{\frac{V_m^2}{2\pi} \int_\alpha^{\pi+\alpha} \sin^2(\omega t) d(\omega t)}$$

$$= \sqrt{\frac{V_m^2}{2\pi} \int_\alpha^{\pi+\alpha} \frac{1 - \cos 2\omega t}{2} d(\omega t)} = \sqrt{\frac{V_m^2}{2\pi} \left[\omega t - \frac{\sin 2\omega t}{2} \right]_\alpha^{\pi+\alpha}}$$

$$= \sqrt{\frac{V_m^2}{4\pi} \left[\left((\pi+\alpha) - \frac{\sin 2(\pi+\alpha)}{2} \right) - \left(\alpha - \frac{\sin 2\alpha}{2} \right) \right]}$$

$$= \sqrt{\frac{V_m^2}{4\pi} \left[\pi + \alpha - \alpha - \frac{\sin(2\pi+2\alpha)}{2} + \frac{\sin 2\alpha}{2} \right]}$$

$$\begin{aligned} &\sin(180+\theta) \\ &= -\sin \theta \end{aligned}$$

$$= \sqrt{\frac{V_m^2}{4\pi} \left[\pi - \left(-\frac{\sin 2\alpha}{2} \right) + \frac{\sin 2\alpha}{2} \right]}$$

$$= \sqrt{\frac{V_m^2}{4\pi} \left[\pi + \frac{2\sin 2\alpha}{2} \right]}$$

$$= \frac{V_m}{2} \sqrt{\frac{1}{\pi} (\pi + \sin 2\alpha)}$$

~~$$= \frac{V_m}{2} \sqrt{1 + \frac{\sin 2\alpha}{\pi}}$$~~

Dimensional
independent

$$V_o \text{ rms} = \frac{V_m}{2}$$

For Half-wave controlled rectifier (R-load)

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v(t)^2 dt}$$


$$V_o \text{ rms} = \sqrt{\frac{1}{2\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t d(\omega t)}$$

$$= \sqrt{\frac{V_m^2}{2\pi} \int_{\alpha}^{\pi} \sin^2 \omega t d(\omega t)}$$

$$= \sqrt{\frac{V_m^2}{2\pi} \int_{\alpha}^{\pi} \frac{1 - \cos 2\omega t}{2} d(\omega t)}$$

$$= \sqrt{\frac{V_m^2}{4\pi} \left[\pi - \frac{\sin 2\pi}{2} - \left(\alpha - \frac{\sin 2\alpha}{2} \right) \right]} = \frac{V_m}{2} \sqrt{\frac{1}{\pi} \left[\pi - \frac{\sin 2\pi}{2} - \alpha + \frac{\sin 2\alpha}{2} \right]}$$

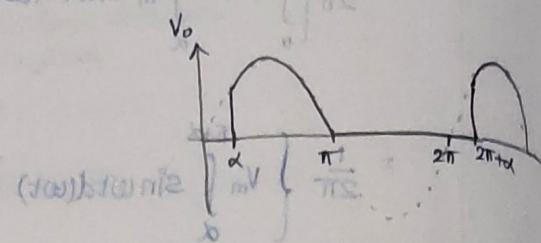
$$V_o \text{ rms} = \frac{V_m}{2\sqrt{\pi}} \sqrt{\pi - \alpha + \frac{\sin 2\alpha}{2}}$$



06-09-2021


Half-wave controlled rectifier

Output for RL load

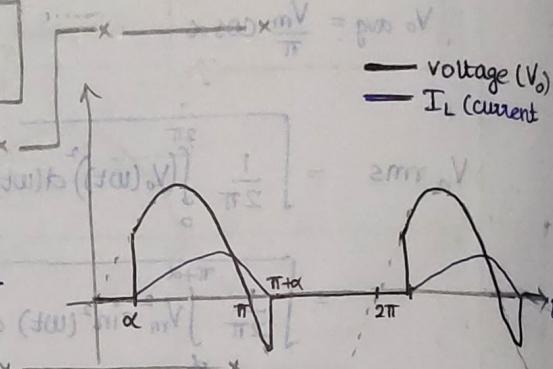


1Φ FULL CONVERTER WITH 'R' LOAD

Bridge circuit

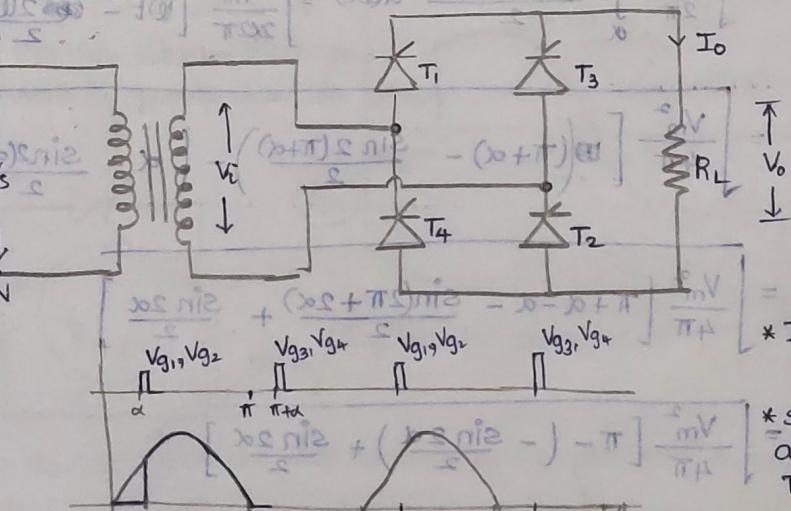


* In +ve half cycle,
T₁ and T₂ conducts

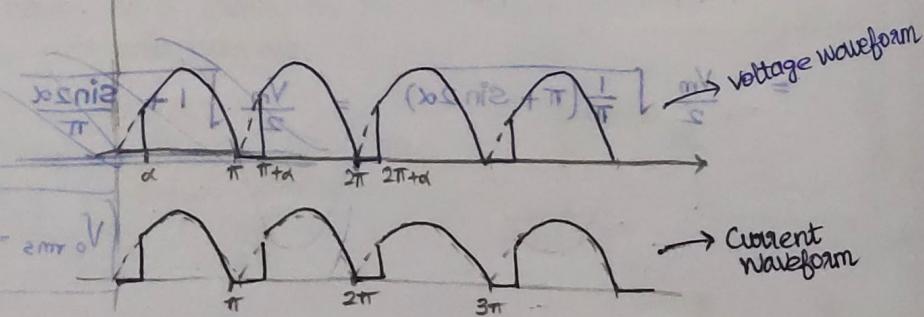* So in +ve half cycle,
apply gate pulse for
T₁ and T₂




In +ve half cycle

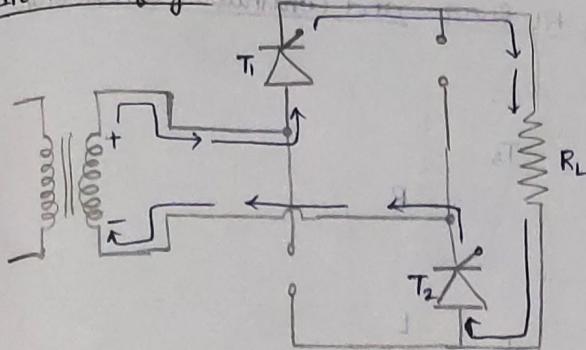

* During +ve half cycle, it is of no use if pulse is given to T_3 and T_4

In -ve half cycle

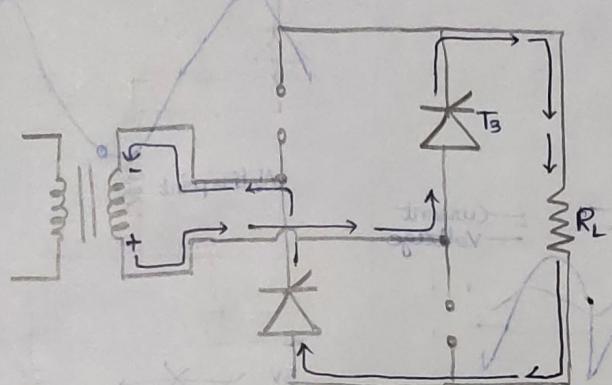

Since, here we have purely resistive load, current & voltage will have same waveform

Here, the output repeats itself for every π

$$V_o \text{ avg} = \frac{\text{Area}}{\text{Base}} = \frac{1}{\pi} \int_{0}^{\pi} V_o d(\omega t) = \frac{1}{\pi} \int_{0}^{\pi} V_m \sin \omega t d(\omega t)$$

$$= \frac{V_m}{\pi} \int_{\alpha}^{\pi} \sin \omega t d(\omega t) = \frac{V_m}{\pi} \left[-\frac{\cos \omega t}{1} \right]_{\alpha}^{\pi}$$

$$= -\frac{V_m}{\pi} [\cos(\pi) - \cos(\alpha)] = -\frac{V_m}{\pi} [-1 - \cos \alpha]$$

$$V_o \text{ avg} = \frac{V_m}{\pi} [1 + \cos \alpha] \Rightarrow I_o \text{ avg} = \frac{V_m}{\pi} [1 + \cos \alpha] \times \frac{1}{R}$$

$$V_o \text{ rms} = \sqrt{\frac{1}{\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t d(\omega t)} = \sqrt{\frac{V_m^2}{\pi} \int_{\alpha}^{\pi} \frac{1 - \cos 2\omega t}{2} d(\omega t)}$$

$$= \sqrt{\frac{V_m^2}{2\pi} \int_{\alpha}^{\pi} (1 - \cos 2\omega t) d(\omega t)} = \sqrt{\frac{V_m^2}{2\pi} \left[\frac{\omega t}{2} - \frac{\sin 2\omega t}{2} \right]_{\alpha}^{\pi}}$$


$$= \sqrt{\frac{V_m^2}{2\pi} \left[\pi - \frac{\sin 2\pi}{2} - (\alpha - \frac{\sin 2\alpha}{2}) \right]} = \sqrt{\frac{V_m^2}{2\pi} \left[\pi - \alpha + \frac{\sin 2\alpha}{2} \right]}$$

$$= \sqrt{\frac{V_m^2}{2\pi} (\pi - \alpha + 0 + \frac{\sin 2\alpha}{2})} = \frac{V_m}{\sqrt{2\pi}} \sqrt{\pi - \alpha + \frac{\sin 2\alpha}{2}}$$

$$V_o \text{ rms} = \frac{V_m}{\sqrt{2\pi}} \sqrt{\pi - \alpha + \frac{\sin 2\alpha}{2}}$$

$$\Rightarrow I_o \text{ rms} = \frac{V_m}{\sqrt{2\pi}(R)} \sqrt{\pi - \alpha + \frac{\sin 2\alpha}{2}}$$

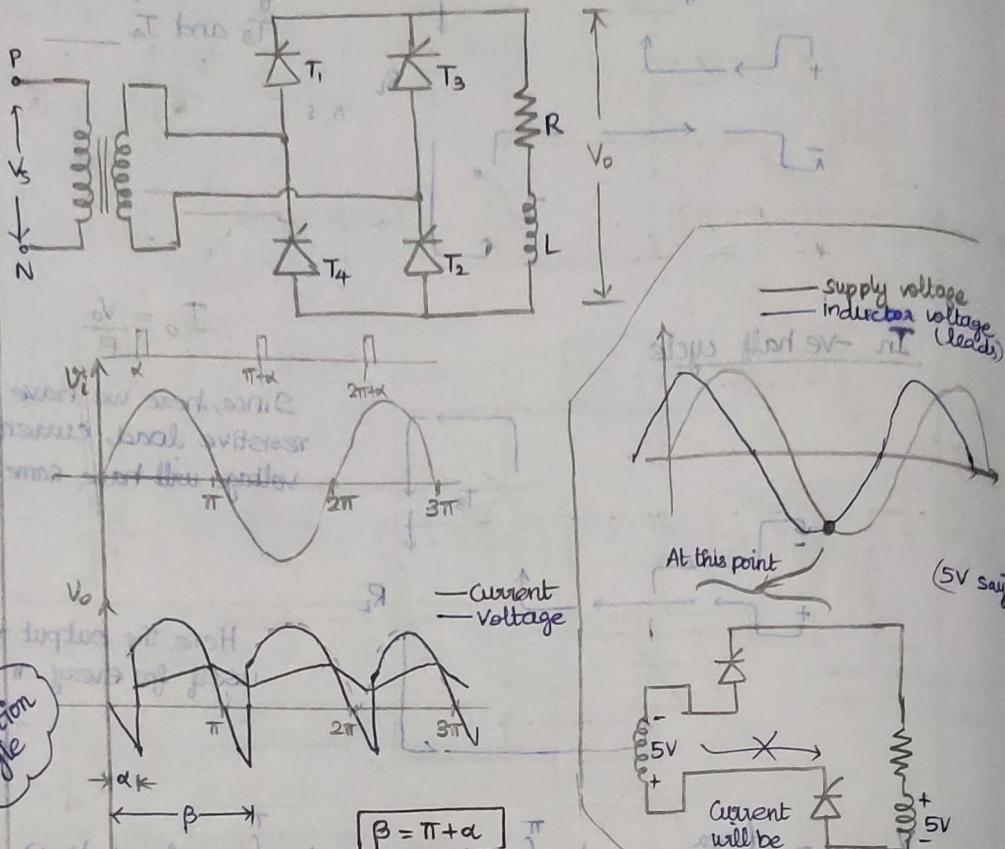1φ Full Converter with RL load and Continuous Conduction



* At any point, the current will not be zero.

* The SCR is triggered before I becomes zero to make the SCR continuously conduct.

* At $-5V$, SCR stops conducting.
* To avoid that, below $-5V$, gate pulse is given.

$$V_{o \text{ avg}} = \frac{1}{\pi} \left[\int_{-\alpha}^{\pi} -V_m \sin \omega t d(\omega t) + \int_{\alpha}^{\pi} V_m \sin \omega t d(\omega t) \right] = \frac{V_m}{\pi} \sin \alpha$$

$$\frac{1}{\pi} \times [2\pi \omega - 1] \frac{mV}{\pi} = 2\pi \omega \cdot I$$

(or)

$$V_{o \text{ avg}} = \frac{1}{\pi} \left[\int_{-\alpha}^{\pi} \left[\int_{-\alpha}^{\pi} V_m \sin \omega t d(\omega t) \right] d(\omega t) \right] = 2\pi \omega \cdot I$$

$$= \frac{V_m}{\pi} \left[\int_{-\alpha}^{\pi} \sin \omega t d(\omega t) \right] = \frac{V_m}{\pi} \left[-\frac{\cos \omega t}{\omega} \right]_{-\alpha}^{\pi}$$


$$= -\frac{V_m}{\pi} \left[\frac{\cos(\pi + \alpha)}{\omega} - \frac{\cos(-\alpha)}{\omega} \right] = -\frac{V_m}{\pi} [\cos \alpha - \cos(\pi + \alpha)]$$

$$V_{o \text{ avg}} = \frac{2V_m \cos \alpha}{\pi}$$

$$\text{When } \alpha = \frac{\pi}{2}, V_{o \text{ avg}} = 0$$


$$\alpha = 90^\circ$$
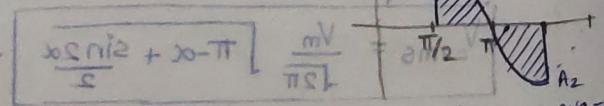
$$\frac{\cos \pi/2 + \cos \pi}{2} = 2\pi \omega \cdot I$$




$$A_1 = A_2 \Rightarrow \text{Avg} = 0$$

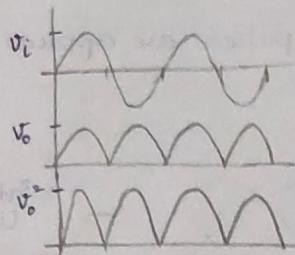* V_o^2 is same as the V_o^2 of full wave uncontrolled rectifier



} full wave uncontrolled rectifier

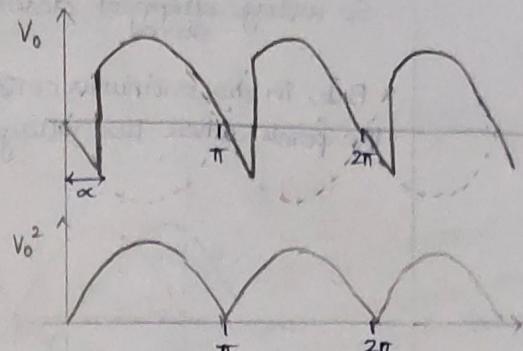

$V_{o\text{ rms}} = V_{o\text{ rms}}$ of full-wave uncontrolled rectifier.


$$V_{o\text{ rms}} = \frac{V_m}{\sqrt{2}}$$

$$80^\circ\text{deg} \times \frac{\pi}{180^\circ\text{deg}} \text{ rad}$$


$$1 \text{ rad} = 180^\circ\text{deg}$$

$$\frac{\pi \text{ rad}}{180^\circ\text{deg}} = 1$$

(08-09-2021)

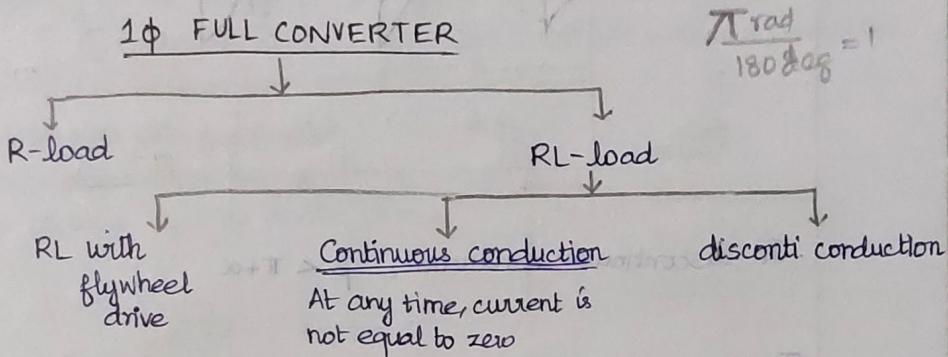

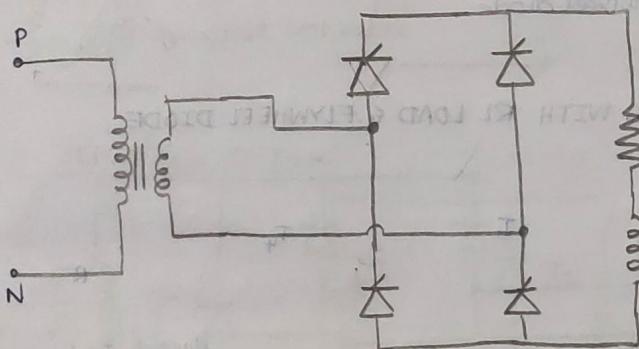1φ FULL CONVERTER WITH RL LOAD - discontinuous conduction




Consider the same ckt as for 1φ full converter with RL load (continuous conduction).

- * In continuous conduction mode, at any point I should not be zero
- * In continuous conduction, when -ve half cycle voltage and inductor voltage are same, I will become zero.
- * To avoid that respective gate pulses ($T_1, T_3 / T_2, T_4$) is given before the point where two voltages are same
- * So current will keep flowing in the circuit.

* But in discontinuous conduction, the inductance value is less, so voltage dropped across it is also less.

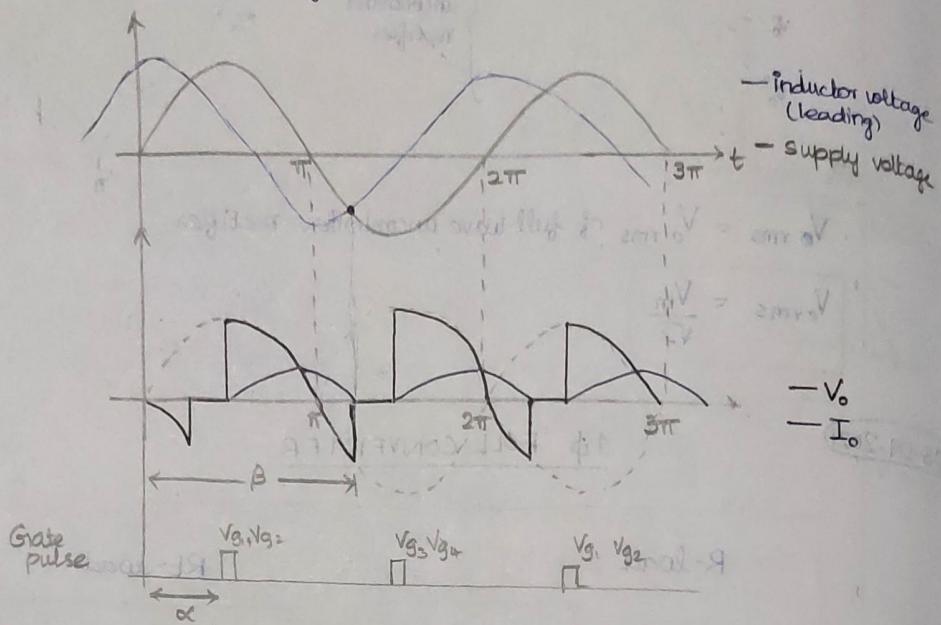
* But, in discontinuous conduction, gate pulses are applied after the points where two voltages are equal.




In discontinuous conduction, $\beta < \pi + \alpha$

Flywheel diode

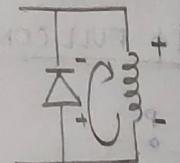→ Stored energy in the inductor is bypassed through the flywheel diode.



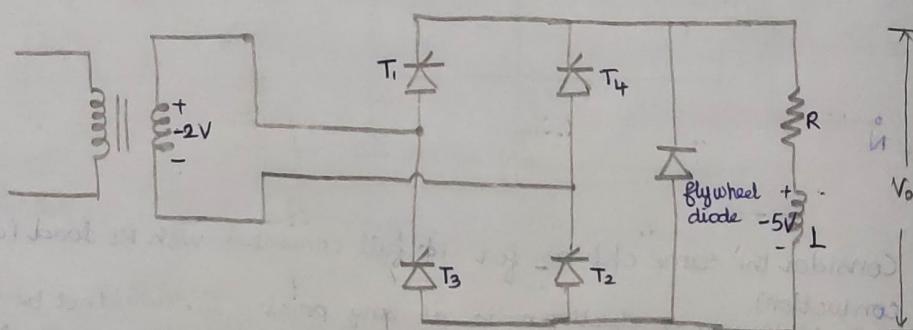1φ - FULL CONVERTER WITH RL LOAD & FLYWHEEL DIODE




* In +ve half cycle, some voltage will be stored in the inductor.


* During negative half cycle, the inductor will discharge in opposite direction.

$$(-5V) > (-2V)$$

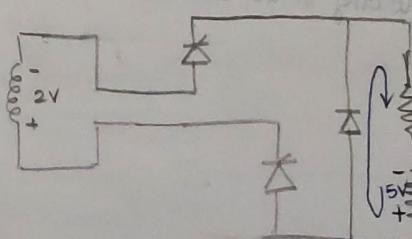(Negative inductance voltage) > (Negative supply voltage)




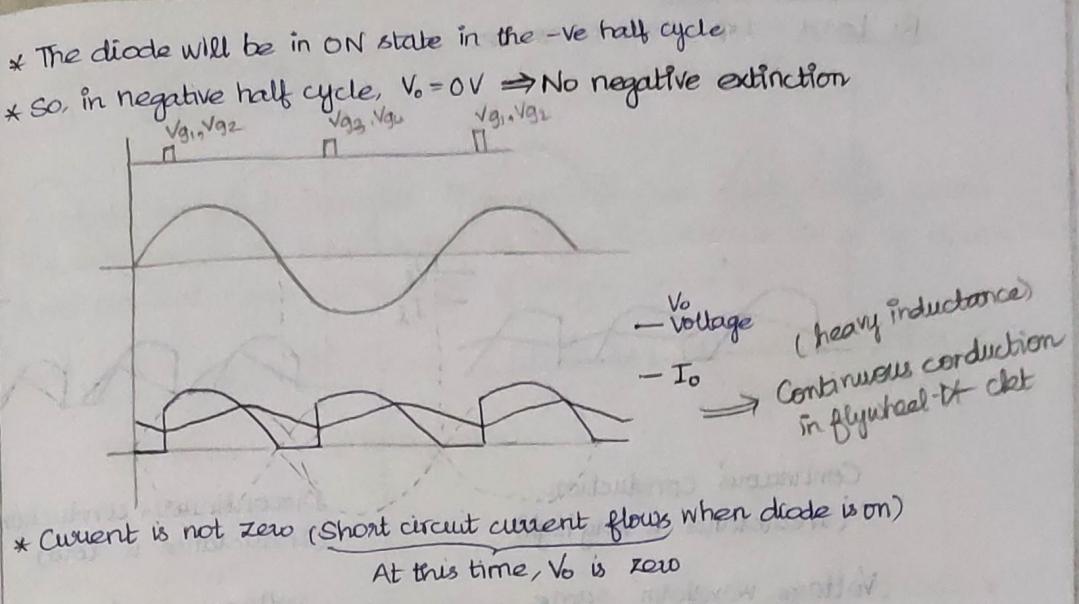When diode is on, it will act like a short circuit




- * In flywheel diode, based on the value of inductance, We can get
 ① Continuous conduction (or) ② Discontinuous conduction

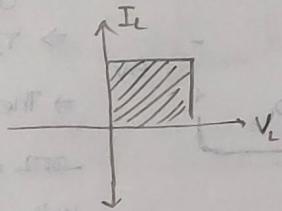- 1φ
 * Full converter with flywheel
 \Rightarrow voltage cannot be -ve
 \Rightarrow current will be positive or zero




One-quadrant converter

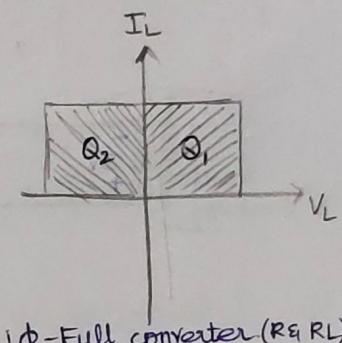


1φ-Full converter ($R \& RL$)
 \Rightarrow voltage (V_o) is +ve & -ve
 \Rightarrow but I_o is always positive or zero

Two-quadrant converter

1φ - SEMI CONVERTER

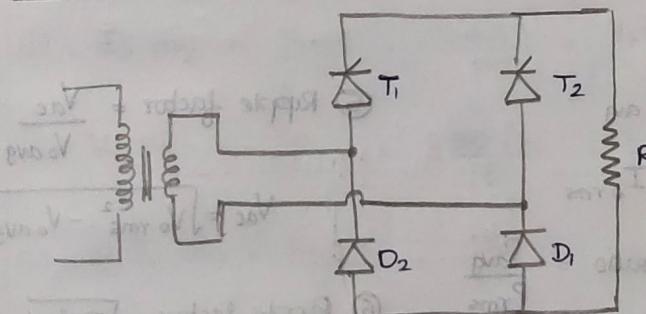

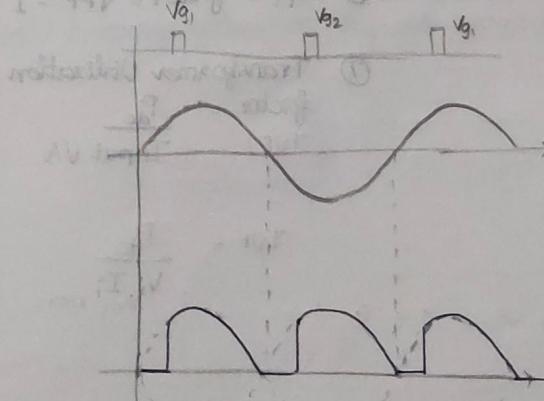There will be one controlled device (SCR) and uncontrolled device (diode) in each paths (forward & backward)




$$V_o \text{ avg} = \frac{V_m}{\pi} [1 + \cos \alpha]$$

$$V_o \text{ rms} = \frac{V_m}{\sqrt{2\pi}} R \sqrt{\pi - \alpha + \sin \frac{\alpha}{2}}$$

V_o avg, V_o rms as same as 1φ - full converter

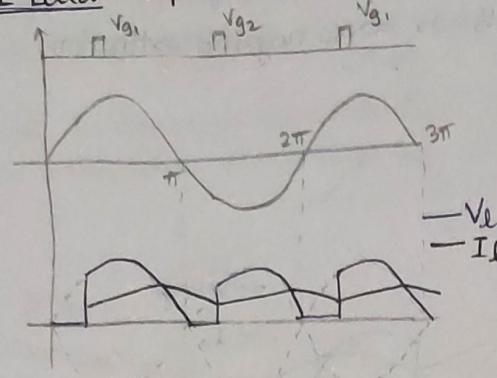
(Inductance is high)
RL Load - 1φ - semi-converter



Continuous conduction
(Inductance is very high)

Voltage waveform same


Current > 0 always

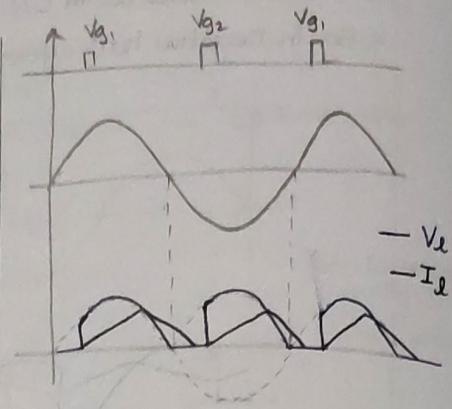

Discontinuous conduction
(Inductance is low)

voltage waveform same

Current > 0 at some time,
current = 0

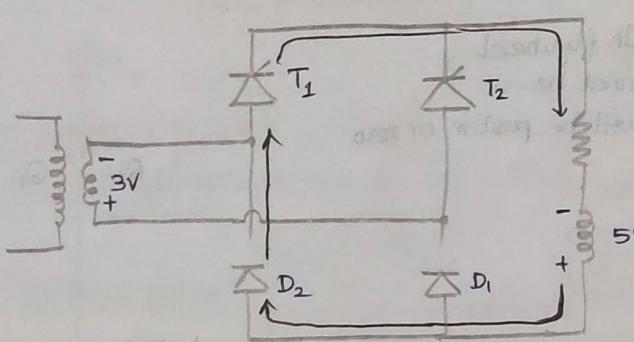

Consider \rightarrow ve half cycle

$\Rightarrow T_1$ was already conducting

$\Rightarrow T_2$ was off

\Rightarrow The shortest path is

$\text{---} \Rightarrow D_2 \Rightarrow T_1 \Rightarrow \text{---}$
not

$\text{---} \Rightarrow D_1 \Rightarrow \text{---} \Rightarrow T_1 \Rightarrow \text{---}$

In \rightarrow ve half cycle, \Rightarrow Negative extinction = 0V

[Voltage across T_1 and D_2 in on state = 0V]
 \Rightarrow acts as flywheel diode

14/09/2021

$$\textcircled{1} P_{dc} = V_o \text{ avg} \times I_o \text{ avg}$$

$$\textcircled{2} P_{o \text{ rms}} = V_{o \text{ rms}} \times I_{o \text{ rms}}$$

$$\textcircled{3} \eta = \text{rectification ratio} = \frac{P_{avg}}{P_{rms}}$$

$$\textcircled{4} \text{ Form factor (FF)} = \frac{V_{o \text{ rms}}}{V_o \text{ avg}}$$

$$\textcircled{5} \text{ Ripple factor} = \frac{V_{ac}}{V_o \text{ avg}}$$

$$V_{ac} = \sqrt{V_{o \text{ rms}}^2 - V_o \text{ avg}^2}$$

$$\textcircled{6} \text{ Ripple factor} = \sqrt{FF^2 - 1}$$

$$\textcircled{7} \text{ Transformer Utilization factor (TUF)} = \frac{P_{dc}}{\text{Input VA}}$$

$$\text{TUF} = \frac{P_{dc}}{V_i I_{i \text{ rms}}}$$

$$\textcircled{8} \text{ Displacement factor } DF = \cos \phi$$

$$\textcircled{9} \text{ PF} = \frac{P_{ac}}{V_{rms} I_{rms}} = \frac{P_{ac}}{\text{Input VA}}$$

① A single phase full converter is supplied from 230V, 50Hz source. The load consists of $R = 20\Omega$ and a large inductance so as to make the load current constant. The firing angle (α) is 45° .

Find (a) $V_o \text{ avg}$ (b) $I_o \text{ avg}$ (c) I_{rms} (d) average value of thyristor current
 (e) V_{rms} (f) Form factor.

Soln

Given $\alpha = 45^\circ$

→ The given voltage is rms voltage. $V_{rms} = 230V \Rightarrow V_m = 230\sqrt{2}V$

→ The inductance is very high (L is very high)


→ Time constant $T = \frac{L}{R}$ is very high

→ Charging & discharging is slow

→ Continuous conduction mode
 → Current is almost constant

Also,
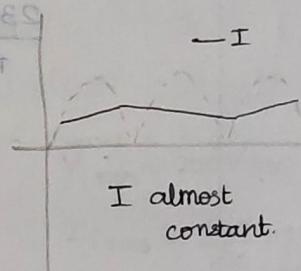
$$\text{since } I_{\text{inductor}} \approx 0 \Rightarrow I \frac{di}{dt} \approx 0$$



I almost constant.

Voltage across inductor = 0V

Soln

$$(a) V_o \text{ avg} = \frac{2 V_m \cos \alpha}{\pi} = \frac{2 \times (230\sqrt{2}) \cos(45^\circ)}{\pi}$$

$$V_o \text{ avg} = 146.42V$$

$$[x \approx 0 + 1] \frac{mV}{\pi} = 146.42V$$


$$(b) I_o \text{ avg} = \frac{V_o \text{ avg}}{R} = \frac{146.42}{20} = 7.32A$$

$$(c) V_o \text{ rms} = \frac{V_m}{(\sqrt{2})(1.0)} = \frac{230\sqrt{2}}{\sqrt{2}} = 230V = \left(1 - \frac{\pi \alpha}{2\pi}\right)$$

$$(c) I_o \text{ rms} = \frac{V_o \text{ rms}}{R} = \frac{230}{20} = 11.5A$$

(d) Average value of thyristor current

$$I_T = I_o \text{ avg}$$

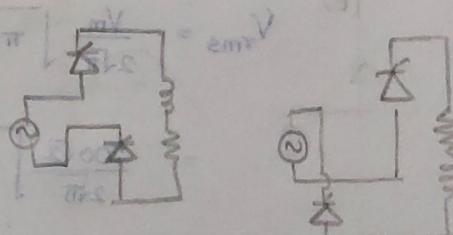

$$\frac{V_o \text{ avg}}{2} + P_{T4.1} - P_{T4.2}$$

$$I_T = \frac{I_o \text{ avg}}{2}$$

(f) Form factor : $\frac{V_o \text{ rms}}{V_o \text{ avg}} = 1.5708$

- ② A single phase full converter is connected to R' load. The source voltage is of 230 V, 50 Hz. The average load current is of 20 A. Find the firing angle. For $R = 10 \Omega$

$$V_o \text{ avg} = \frac{V_m}{\pi} [1 + \cos \alpha]$$

1φ full converter
R-load

Also $I_o \text{ avg} = \frac{V_o \text{ avg}}{R} \Rightarrow \frac{V_o \text{ avg}}{R} = 20$

$$\Rightarrow V_o \text{ avg} = 20 \times R$$

$$V_o \text{ avg} = 200$$

$$\frac{230\sqrt{2}}{\pi} [1 + \cos \alpha] = 200 \Rightarrow 1 + \cos \alpha = 1.931$$

$$\cos \alpha = 0.931 \Rightarrow \alpha = 0.3736 \text{ rad}$$

$$\alpha = 21.40^\circ$$

- ③ A single phase HW controlled rectifier is operated from 200 V, 50 Hz supply. If the R_L is 100Ω and average output voltage is 50 V.

Find (a) α (b) $V_{o \text{ rms}}$, (c) $I_{o \text{ rms}}$ (d) FF (e) RF (f) TUF

Soln

(a) $V_o \text{ avg} = \frac{V_m}{2\pi} [1 + \cos \alpha]$ Given $V_o \text{ avg} = 50 \text{ V}$

$$\Rightarrow \frac{1}{50} = \frac{200\sqrt{2}}{2\pi} [1 + \cos \alpha] \quad V_m = 200\sqrt{2} \quad (d)$$

$$\left(\frac{2\pi}{4\sqrt{2}} - 1 \right) = \cos \alpha \Rightarrow \alpha = \cos^{-1}(0.1107) = 1.459 \text{ rad} \quad (d)$$

$$\alpha = 83.64^\circ$$

(b) $V_{o \text{ rms}} = \frac{V_m}{2\sqrt{\pi}} \sqrt{\pi - \alpha + \frac{\sin 2\alpha}{2}}$

$$= \frac{200\sqrt{2}}{2\sqrt{\pi}} \sqrt{\pi - (1.459) + \frac{\sin(2 \times 1.459)}{2}}$$

$$= \frac{200\sqrt{2}}{2\sqrt{\pi}} \sqrt{3.14 - 1.459 + \frac{0.22}{2}}$$

RAD mode

$$\sin(2 \times 1.459) = 0.22$$

DEG MODE

$$\sin(2 \times 83.64) = 0.22$$

$$V_{o\text{rms}} = \frac{200\sqrt{2}}{2\sqrt{\pi}} \sqrt{1.791}$$

$$\text{Now } V_o = \frac{100\sqrt{2}}{\sqrt{\pi}} \times 1.3382$$

$$V_{o\text{rms}} = 106.772 \text{ V}$$

$$\pi \text{ radians} = 180^\circ$$

deg to radians conversion

$$\text{rad} = \frac{(\text{deg})}{180^\circ/\text{deg}} \times 3.14 \text{ rad}$$

$$(c) I_{o\text{rms}} = \frac{V_{o\text{rms}}}{R} = \frac{106.772}{100} = 1.0677 \text{ A}$$

$$(d) FF = \frac{V_{o\text{rms}}}{V_{o\text{avg}}} = \frac{106.772}{50} = 2.13544$$

$$(e) \text{Rectification factor} = \frac{P_{\text{avg}}}{P_{\text{rms}}} = \frac{V_{o\text{avg}} I_{o\text{avg}}}{V_{o\text{rms}} I_{o\text{rms}}} = \frac{50 \times \left(\frac{50}{100}\right)}{106.772 \times 1.0677}$$

$$= \frac{25}{114.0025} = 0.2192$$

$$(f) \text{TUF} = \frac{P_{dc}}{V_{o\text{rms}} I_{o\text{rms}}} = \frac{V_{o\text{avg}} \times I_{o\text{avg}}}{200 \times 2} \quad V_{o\text{rms}} = 200 \text{ V (ac)}$$

$$I_{o\text{rms}} = \frac{200}{100} = 2 \text{ A (ac)}$$

$$= \frac{V_{o\text{avg}} \times I_{o\text{avg}}}{106.772 \times 1.0677}$$

$$= \frac{50 \times \left(\frac{50}{100}\right)}{(200 \times 2)} = \frac{25}{400} = 0.0625$$


- ④ In a single phase full converter all thyristors are given constant dc voltage. The load is of R type. Draw output voltage and find $V_{o\text{avg}}$.

Soln

When constant dc voltage is given to thyristor (gate of thyristor), then all thyristors will be on when they are forward biased.

Then α will be zero

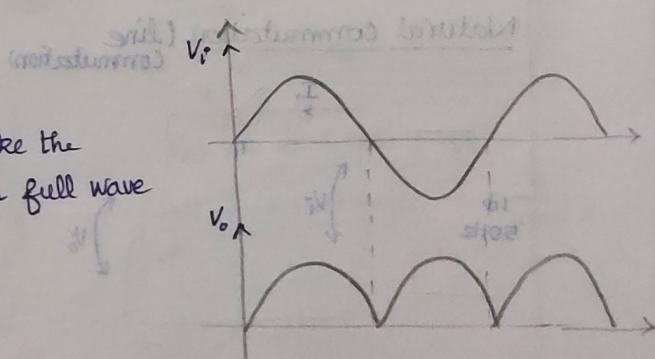
The output voltage will be like the output voltage of uncontrolled full wave rectifier



for first half AC phase 2A in
on - off lossless switch if no load
(slope flat)

because of this resistance losses in a

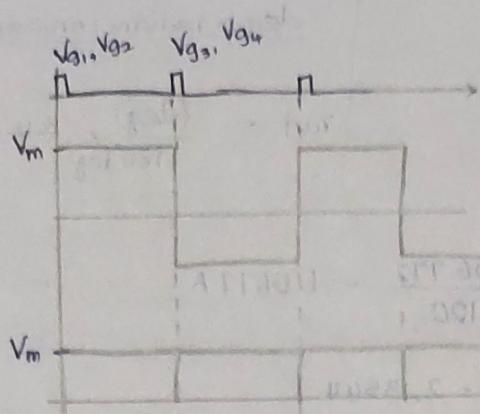- ⑤ In a full converter with 'R' load the thyristor is triggered at $\alpha=0$ and input is a square wave. Find V_o ?



The output is a dc waveform.

Aug 25
2021

- (1d)
- ⑥ In a full converter when $\alpha=0^\circ$, the output voltage is 300V. The load is RL type and continuous conduction. ~~Find V_o avg for $\alpha=60^\circ$~~ . Find V_o avg for $\alpha=60^\circ$.
- ⑦ A 1φ HWR is fired at α . If the peak value of the instantaneous output equals 230V. Find α when $V_i = 230V$.

In
asym

Aug 23 $\frac{0.5}{300} = \text{emi } I$

COMMUTATION CIRCUIT


The process of turning off the conducting SCR (thyristor) is called commutation.

Commutation

(5) x 02


- Natural commutation (for ac supply)
- Forced commutation (for dc supply)
 - Load commutation or self commutation (or resonant)
 - current or resonant pulse.
- complementary
- Voltage (or) impulse
- External pulse commutation

Natural commutation (line commutation)

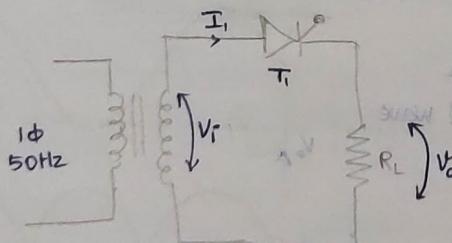


In AC Supply SCR will turn off by itself when it is reverse biased (by -ve half cycle)

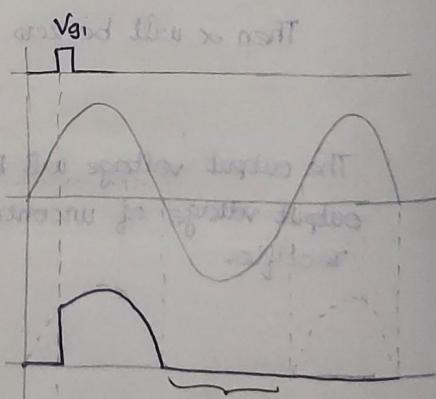* No external commutation circuit is needed.




SCR turned off by itself due to rev. bias

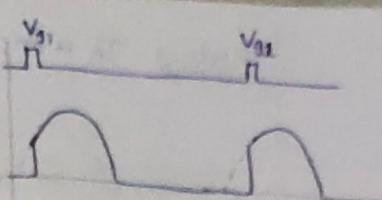- * If gate pulse is applied periodically,
- * for each cycle, diode needs to be triggered in ac supply



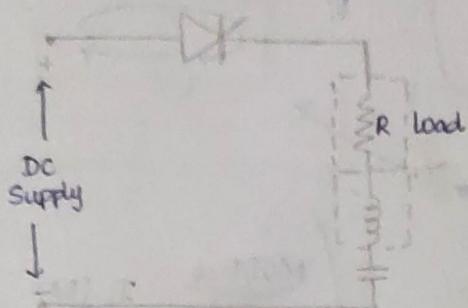
Load Commutation (on) Resonant commutation (on) self commutation




* R and L are the load

* L and C are the commutating components

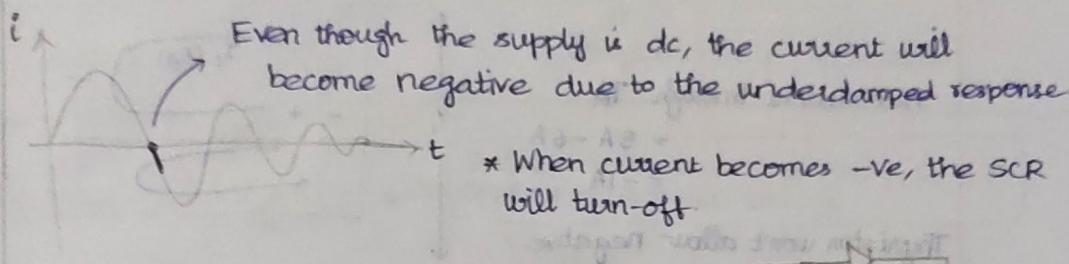
* In RLC circuit, when $X_L < X_C$,
We get underdamped response



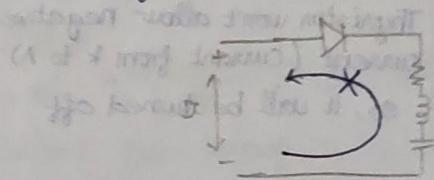* When current becomes -ve, the SCR will turn-off




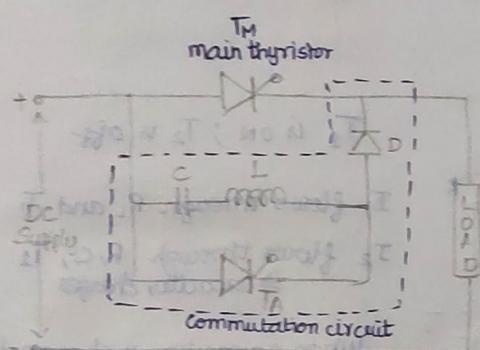Current Commutation (Class B commutation)



T_A - auxiliary thyristor


Mode-1 T_M is off ; T_A is off

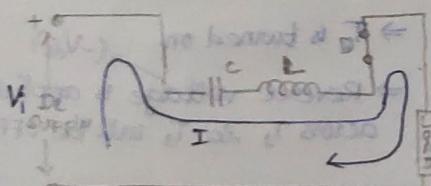

Capacitor will start charging to V_i volts.

After capacitor starts, I becomes zero



Mode-2 T_M is on ; T_A is off

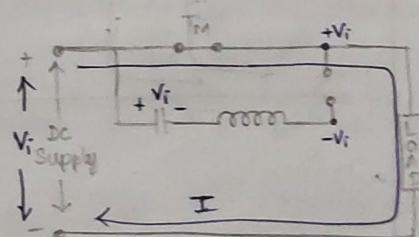

$V_{AK} < 0 \Rightarrow$ Diode is off

Now I is constant $I = \frac{V_i}{Load\ R}$

Mode-3 T_A is on; T_M is ON

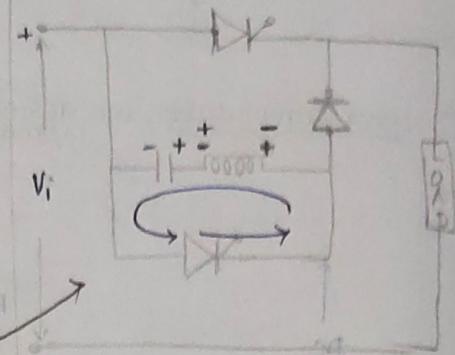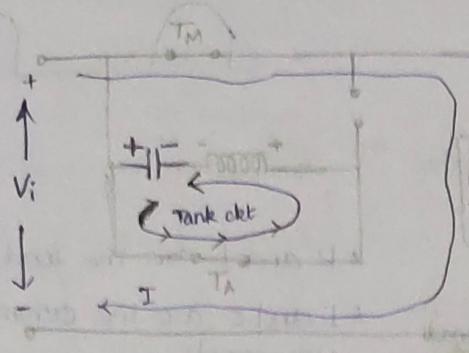

*Capacitor will charge inductor.

Inductor will again charge the capacitor.


Net current through T_M

$$= 5A - 6A \\ = -1A$$

Thyristor won't allow negative current (current from k to A)

so, it will be turned off


MODE-4 $I_1 (5A)$

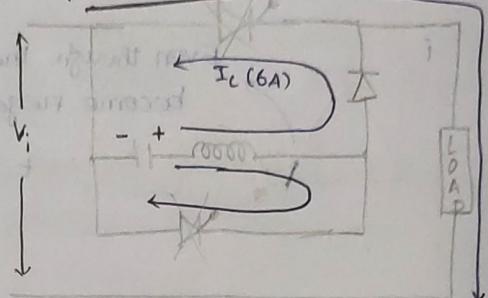

\Rightarrow capacitor current will turn off both T_M and T_A . Hence commutation is performed.

Complementary Commutation

switching sequence - AT

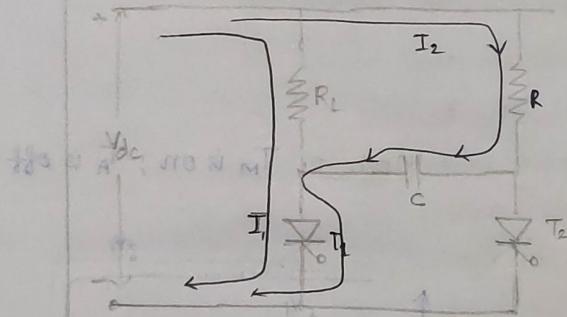

T_1 is ON ; T_2 is off

I_1 flows through R_L and T_1

I_2 flows through R, C, T_2 \Rightarrow capacitor charges

When capacitor is charged

$$V_c = V_{dc} \Rightarrow I_2 = 0$$


goes at AT ; go to AT

$\Rightarrow T_2$ is turned on $(-V_{dc})$

\Rightarrow Reverse voltage is applied across T_1 so T_1 will be OFFed.

process goes like this


current I_1 starts with $5A$

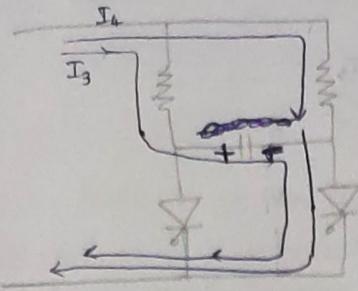

Capacitor charges in opposite direction

$$R_L \rightarrow C \rightarrow T_2 \rightarrow I_3$$

$$R \rightarrow T_1 \rightarrow I_4$$

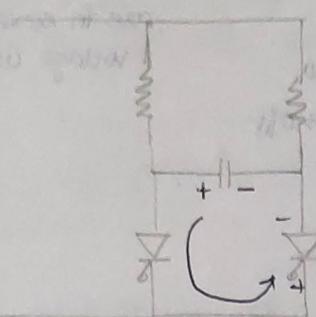

Turn on $T_1 \Rightarrow T_2$ will be turned off
(due to reverse voltage)

To turn off T_2 , turn on T_1


To turn off T_1 , turn off T_2

↓
Complementary commutation

VOLTAGE COMMUTATION

Sudden reverse voltage across SCR is applied \Rightarrow SCR will turn off

Mode-1

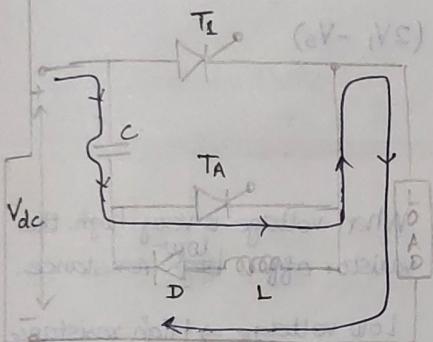

T_A is on. T_1 is off

\Rightarrow Current flows through C , T_A , Load.

\Rightarrow This current charges the capacitor C .

When $V_C = V_{dc}$ (capacitor charged),

$I = 0 \Rightarrow T_1$ will turn off



Mode-2 (T_A is in off condition)

* T_1 is turned on by giving gate pulse

* The capacitor charges the inductor

(Tank circuit)

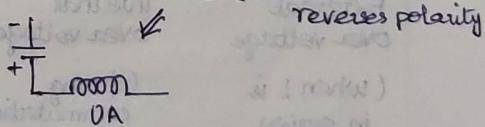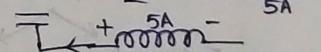* Next time inductor charges the capacitor




(reverses polarity)


Mode-3

* When T_A is turned ON, T_A conducts and

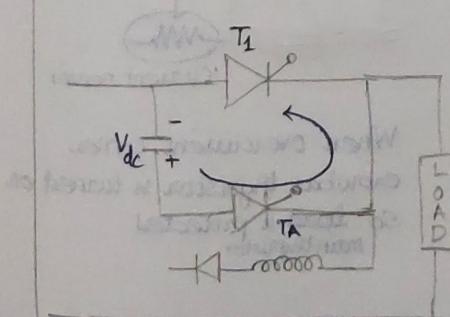$V_{AK} = -V_{dc} \Rightarrow T_1$ will be turned off



EXTERNAL PULSE COMMUTATION (CLASS-E)

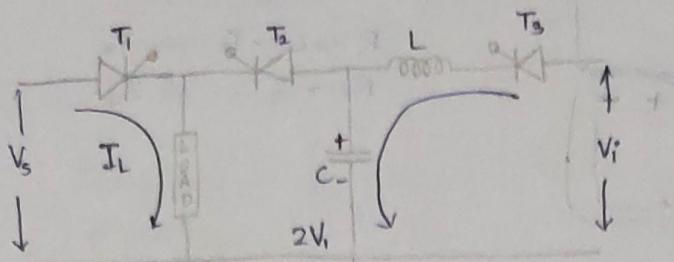


Step-I : Turn on T_1 and T_3

once capacitor is charged, I becomes zero,

T_3 turns off

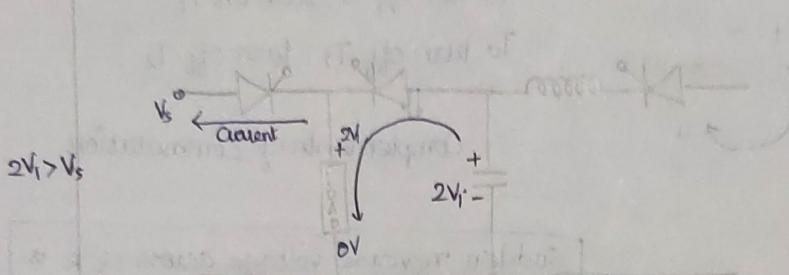When L & C are in series,
voltage will be doubled.



Step-II : To turn off T_1 , turn ~~on~~ T_2

$$V_{AK} \text{ of } T_1 = (2V_i - V_s)$$

$V_{AK} > 0 \Rightarrow T_1$ will be OFFed.


THYRISTOR PROTECTION

- (1) Over voltage protection
- (2) Over current protection
- (3) $\frac{dv}{dt}$ protection
- (4) $\frac{di}{dt}$ protection
- (5) Gate protection

① Over Voltage Protection

External over voltage
(when L is in series)
internal over voltage
(during commutation)

Varistor

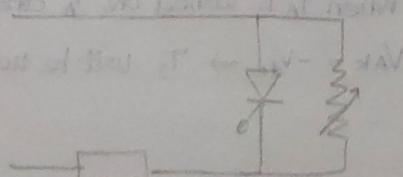


When voltage is very high, the varistor offers ~~low~~ resistance.

Low voltage \Rightarrow High resistance


② Over current protection

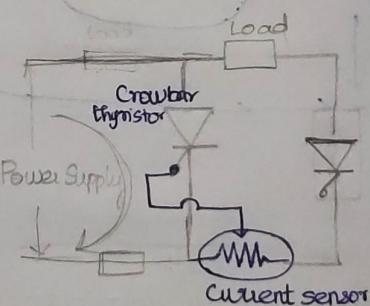- * We can use
 - \Rightarrow FACL fuse
(fast acting current limiter)
 - \Rightarrow Electronic Crowbar Protection




When overcurrent comes, crowbar thyristor is turned on. So ~~load~~ is protected main thyristor

③ $\frac{dv}{dt}$ protection

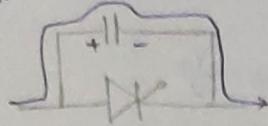


When high $\frac{dv}{dt}$ comes, capacitor will act as a short circuit and also it will start charging.

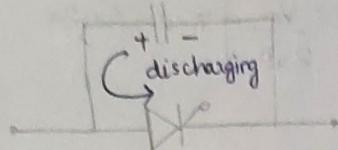Then it will discharge after the high $\frac{dv}{dt}$ goes



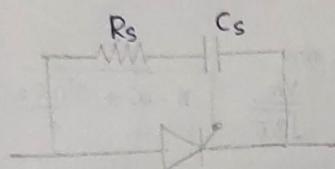To avoid this, we have a resistor in discharge path



"Snubber Protection"

Uncontrolled rectifiers

Half-wave

$$V_o \text{ avg} = \frac{V_m}{\pi}$$

$$V_o \text{ rms} = \frac{V_m}{2}$$

Full-wave

$$V_o \text{ avg} = \frac{2V_m}{\pi}$$

$$V_o \text{ rms} = \frac{V_m}{\sqrt{2}}$$

Controlled rectifiers

Half-wave
(R load)

$$V_o \text{ avg} = \frac{V_m}{2\pi} (1 + \cos \alpha)$$

$$V_o \text{ rms} = \frac{V_m}{2\sqrt{\pi}} \sqrt{\pi - \alpha + \frac{\sin 2\alpha}{2}}$$

Half-wave
(RL load)

$$V_o \text{ avg} = \frac{V_m}{\pi} \cos \alpha$$

$$V_o \text{ rms} = \frac{V_m}{\sqrt{2}\pi} \sqrt{1 + \frac{\sin 2\alpha}{2}}$$

Full-wave
(R load)

$$V_o \text{ avg} = \frac{V_m}{\pi} [1 + \cos \alpha]$$

$$V_o \text{ rms} = \frac{V_m}{\sqrt{2}\pi} \sqrt{\pi - \alpha + \frac{\sin 2\alpha}{2}}$$

Full-wave
(RL load)

$$V_o \text{ avg} = \frac{2V_m}{\pi} \cos \alpha$$

$$V_o \text{ rms} = \frac{V_m}{\sqrt{2}}$$

$$\textcircled{1} P_{dc} = I_{avg} \times V_{avg}$$

$$\textcircled{6} \text{ Ripple factor} = \sqrt{FF^2 - 1}$$

$$\textcircled{2} P_{rms} = V_{rms} \times I_{rms}$$

$$\textcircled{7} TUF = \frac{P_{dc}}{\text{Input VA}} = \frac{P_{dc}}{V_{rms} I_{rm}}$$

$$\textcircled{3} \text{ Rectification ratio} = \eta = \frac{P_{avg}}{P_{rms}}$$

$$\textcircled{8} \text{ Displacement factor} = \cos \phi$$

$$\textcircled{4} \text{ Form factor} = \frac{V_{rms}}{V_{avg}}$$

$$\textcircled{9} PF = \frac{P_{ac}}{\text{Input VA}}$$


$$\textcircled{5} \text{ Ripple factor} = \frac{V_{ac}}{V_{avg}}$$

$$V_{ac} = \sqrt{V_{rms}^2 - V_{avg}^2}$$

DC - DC Converter (DC chopper)

Oct 4

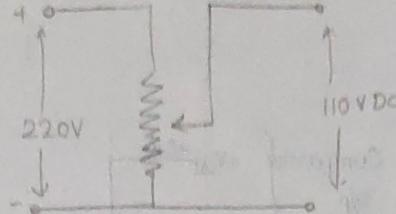
- * Converts fixed DC to variable DC
 - * also known as DC transformer
 - * a conventional ^{fixed} DC - variable DC converter is a voltage divider (resistor)
- Application:- Traction motor control, marine hoists, mine haulers



Disadvantage of potential divider:


- * Wastage of electrical energy

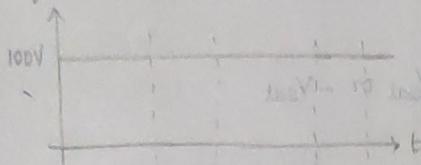✓ **DC choppers** - Chops (cuts the DC Waveform)



$$T = T_{ON} + T_{OFF}$$

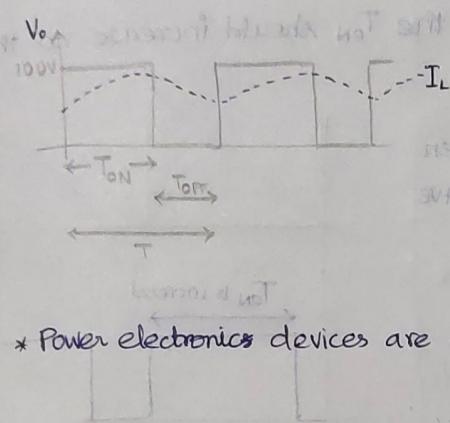- * Due to inductance present in the load, current will be continuous (similar to triangular wave)



- * Power consumed during T_{OFF} time

$$= V_o \times I_L = 0W$$

$$\text{Duty Cycle } K = \frac{T_{ON}}{T}$$


in some books
 α is duty cycle

- * Power electronics devices are energy efficient (very low or no wastage of energy)

Oct 5
[offline]

Basic chopper

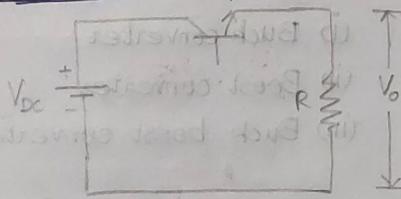Transistor will operate only on saturation region or cut-off region (OFF)



$$V_{avg} = \frac{\text{Area}}{\text{Base}} = \frac{V_{dc} \times T_{ON}}{T}$$


$$V_{avg} = \alpha V_{dc}$$

since $\alpha = \frac{T_{ON}}{T}$
duty cycle

$$V_{rms} = \sqrt{\frac{V_{dc}^2 \times T_{ON}}{T}} = \sqrt{\alpha} V_{dc}$$

$$V_{rms} = \sqrt{\alpha} V_{dc}$$
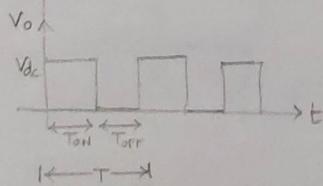
$$\text{effective i/p resistance} = R_i = \frac{R}{\alpha}$$



✓ **T-chopping Frequency**


Modes of Control

(i) Constant frequency control (T is constant; T_{ON} or T_{OFF} is varied)

Width of pulse is varied
⇒ pulse width modulation

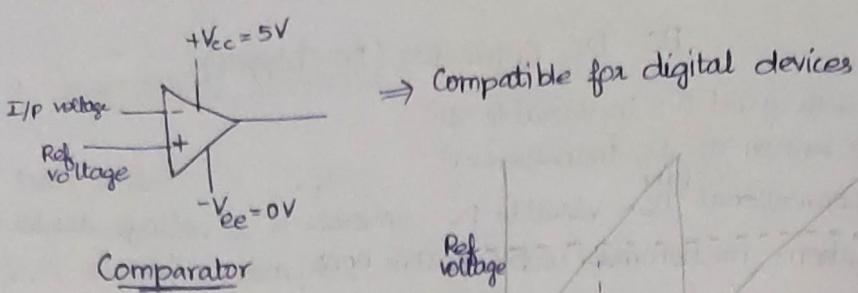(ii) Variable frequency control (T is not constant; T_{ON} or T_{OFF} is constant)

frequency modulation
⇒ generate unpredictable harmonics (filter design is difficult)



Comparator o/p voltage
 $= (V^+ - V^-) \times A_{OL}$

But when the I/P exceeds, $+V_{sat}$ or $-V_{sat}$, then o/p voltage will be $+V_{sat}$ or $-V_{sat}$

If we increase the ref. voltage, the T_{on} should increase so that V_{avg} increases.


So, ref. voltage should be given to -ve terminal & I/P voltage to +ve terminal

Types of Converters (Choppers)

(i) Step-up chopper $\Rightarrow V_o > V_{in} \Rightarrow$


(ii) Step-down chopper
 $\Rightarrow V_o < V_{in} \Rightarrow \alpha < 0.99$

Step-up chopper

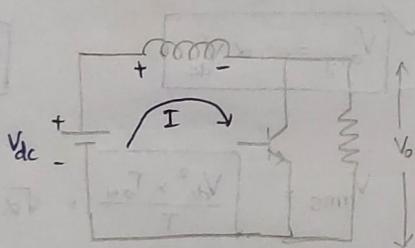


Inductor charges when Transistor is on. $\Rightarrow V_o = 0V$

When transistor turns off

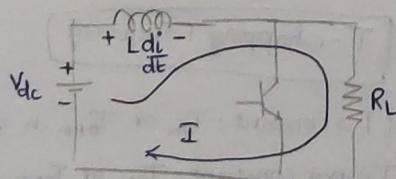


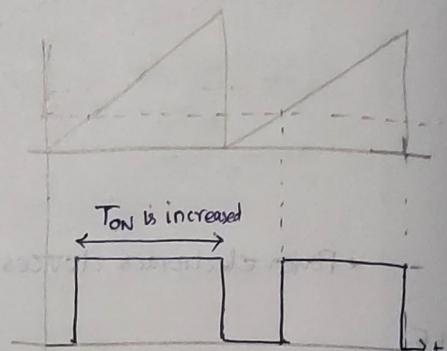
$$V_o = V_{dc} + \frac{L}{R_L} \frac{di}{dt} \text{ Volts}$$



- (i) Buck converter
- (ii) Boost converter
- (iii) Buck boost converter

* Higher the switching frequency, lesser the value of ripples.

Buck Converter

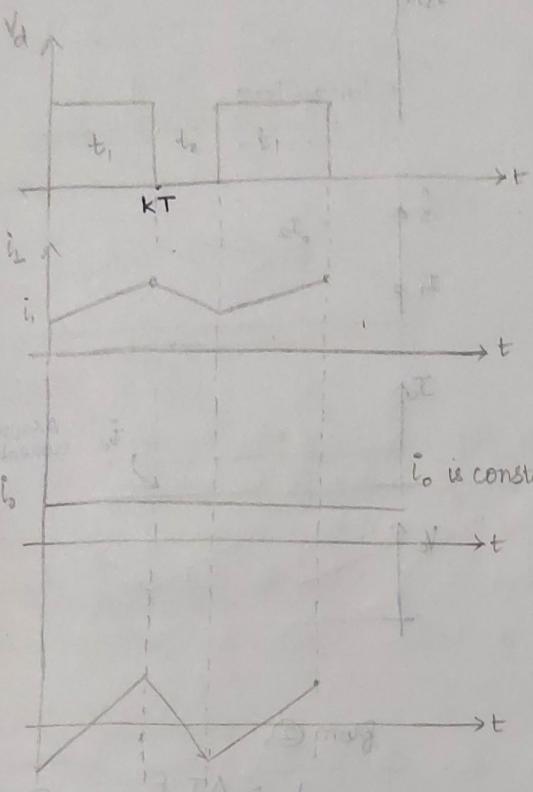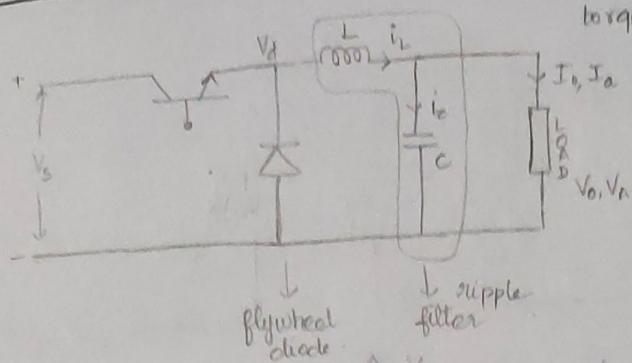

$$e_L = L \frac{di}{dt}$$

$$V_s - V_a = \frac{L (I_2 - I_1)}{t_1}$$

$$= \frac{L \Delta I}{t_1}$$

$$t_1 = \frac{\Delta I \cdot L}{V_s - V_a} \rightarrow \textcircled{A}$$


$$\boxed{\Delta I = \frac{t_1 (V_s - V_a)}{L}} \rightarrow \textcircled{1}$$

I_L falls at t_2

$$0 - V_a = \frac{L (I_1 - I_2)}{t_2}$$

$$\boxed{t_2 = \frac{\Delta I \cdot L}{V_a}} \rightarrow \textcircled{B}$$

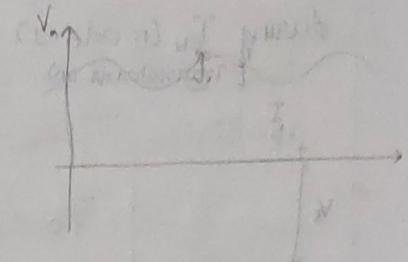If the voltage is given to motor, it will have fluctuating torque, to avoid that, the voltage must be flattened.



$$\begin{aligned} t_1 (V_s - V_a) &= \frac{t_2 V_a}{L} \\ (t_1 + t_2) V_s &= t_1 V_a + t_2 V_a \\ t_1 V_s &= (t_1 + t_2) V_a \end{aligned}$$

$$\frac{T_2}{T_1} = \frac{1 - k}{k}$$

$$\Delta I = \frac{t_2 V_a}{L} \rightarrow \textcircled{2}$$

equating \textcircled{1} & \textcircled{2},

$$V_a = \frac{V_s \cdot t_1}{T} = k V_s$$

$$T = t_1 + t_2 = \frac{\Delta I \cdot V_s}{V_a (V_s - V_a)}$$


$$L = \frac{V_s \cdot k (1 - k)}{\Delta I \cdot f} \quad (\because f = \frac{1}{T})$$

$$\Delta V_c = \frac{1}{C} \int_0^{T/2} \Delta I / 4 \, dt$$



$$\boxed{C = \frac{\Delta I}{\Delta V_c \cdot 8f}}$$

October 7
Offline



II Boost Converter

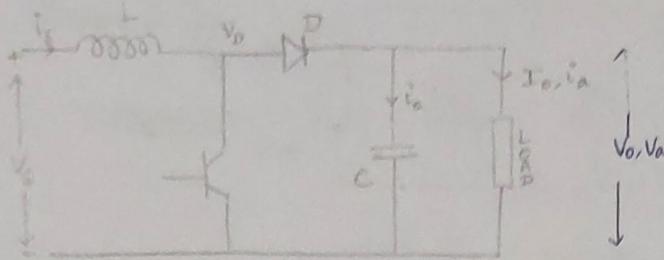

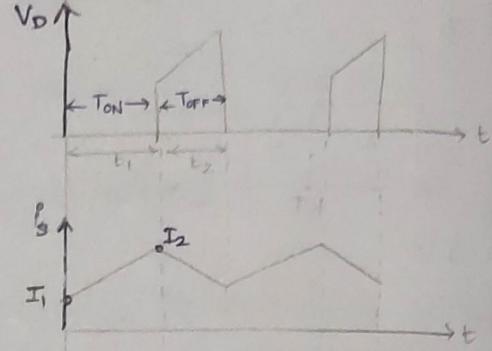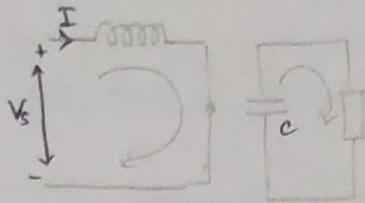during T_{ON} (mode-I)
[Transistor is on]



during T_{OFF} (mode-II)

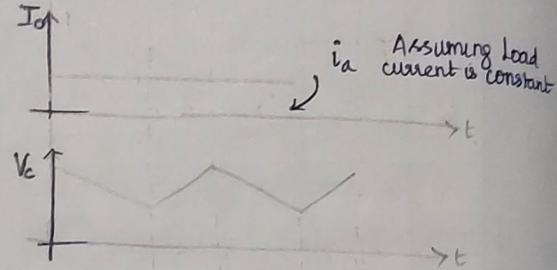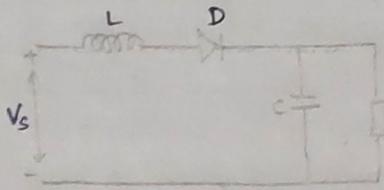

$$e = L \frac{dI}{dt}$$

during T_{ON}

$$V_s = L \frac{(I_2 - I_1)}{t_1} \Rightarrow t_1 = \frac{\Delta I \cdot L}{V_s}$$

$$V_s = \frac{L \Delta I}{t_1} \Rightarrow \Delta I = \frac{V_s t_1}{L} \rightarrow ①$$

from ②,

$$L = \frac{\Delta I \cdot f}{V_s k} \rightarrow ④$$

$$\Delta V_c = \frac{1}{C} \int_0^{t_1} I_c \cdot dt$$

$$= \frac{1}{C} I_a t_1$$

during t_2 (T_{OFF})

$$V_s - V_a = -\frac{L \Delta I}{t_2} \Rightarrow t_2 = \frac{\Delta I \cdot L}{V_a - V_s}$$

$$C = \frac{f \cdot \Delta V_c}{I_a k} \rightarrow ⑤$$


$$\Delta I = \frac{t_2 (V_a - V_s)}{L} \rightarrow ②$$

Comparing ① & ②,



$$V_a = \frac{V_s T}{t_2} = \frac{V_s}{1-k}$$

→ ③



III Buck-Boost Converter

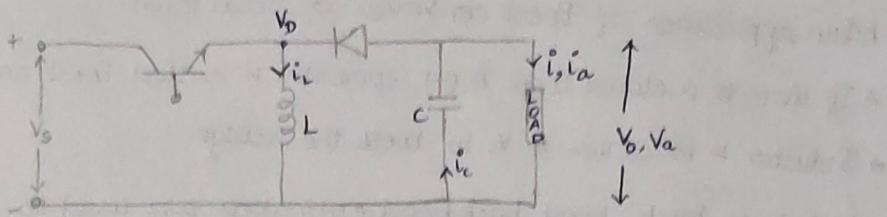

during T_{ON} (mode-I)

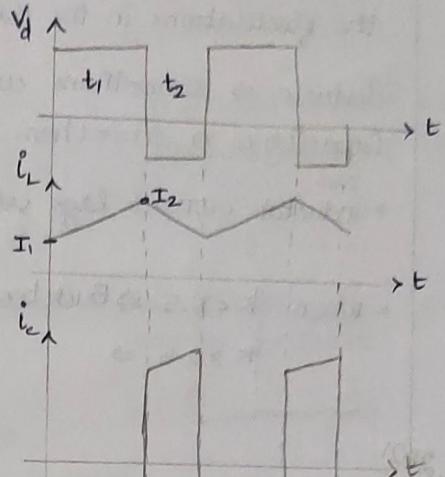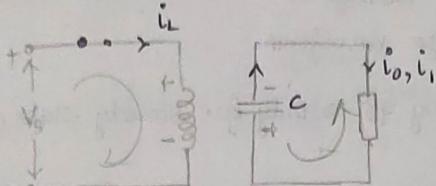

during T_{OFF} (mode-II)

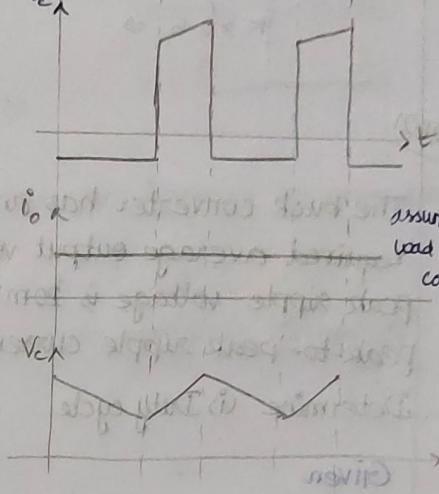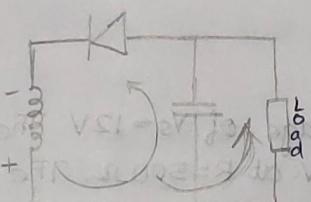

assuming load current is constant

during t_1

$$V_s = \frac{L \cdot \Delta I}{t_1} \Rightarrow t_1 = \frac{\Delta I \cdot L}{V_s} \rightarrow \textcircled{A}$$

from ① & ②

$$V_a = \frac{V_s \cdot k}{1 - k}$$

$$\Delta I = \frac{V_s \cdot t_1}{L} \rightarrow \textcircled{1}$$

$$I_d = \frac{V_s \cdot k}{\Delta I \cdot f}$$

during t_2

$$V_a = -L \frac{\Delta I}{t_2}$$

$$C_L = \frac{f \cdot \Delta V_c}{I_a \cdot k}$$

$$t_2 = -\frac{\Delta I \cdot L}{V_a} \rightarrow \textcircled{B}$$

$$\Delta I = -\frac{V_a t_2}{L} \rightarrow \textcircled{2}$$

* Solar panel is a current source. Voltage will not be constant due to variation in sunlight.

Main application of Boost converter \Rightarrow Solar Panel

* If there is a closed loop, boost converter is called boost controller.

* Inductor is in series to V_s to boost the voltage.

* L & C in buck, boost, buck-boost converters are used to filter out the fluctuations in the output power.

Inductor \Rightarrow smoothes current waveform

Capacitance \Rightarrow smoothes voltage waveform

* ^{pure} inductor current lags voltage by 90° \Rightarrow only for steady state conditions

* When $k < 0.5 \Rightarrow$ Buck-boost will act as buck

$k > 0.5 \Rightarrow$ act as boost

$5 \times 2 = 10 \Rightarrow$ Under

$2 \times 10 = 20 \Rightarrow$ Apply

Oct 11, 2021
 The buck converter has an input voltage of $V_s = 12V$. The required average output voltage is 5V. at $R = 500\Omega$. The peak-to-peak ripple voltage is 20mV. The switching frequency is 25kHz. If the peak-to-peak ripple current of inductor is limited to 0.8 A.

Determine (i) Duty cycle (ii) Filter inductance (iii) Filter Capacitance

Given

$$V_s = 12V ; V_o = 5V \text{ DC} ; \Delta V = 20mV ; \Delta I_o = 0.8A ; R = 500\Omega ; f = 25 \text{ kHz}$$

Buck Converter,

$$* V_o = k V_s \Rightarrow k = \frac{V_o}{V_s} = \frac{5}{12} = 0.416 \Rightarrow \boxed{k = 0.416}$$

$$* L = \frac{V_s k (1-k)}{\Delta I \cdot f} = \frac{12 \times 0.416 (1-0.416)}{0.8 \times 25000} = \frac{2.9153}{20,000}$$

$$= 1.457 \times 10^{-4} \times \frac{10}{10} \boxed{L = 0.1457 \text{ mH}} = 145.7 \mu\text{H}$$

$$* C = \frac{\Delta I}{\Delta V \times 8f} = \frac{2 \times 10^{-4} \times 10}{10} = 0.2 \text{ mF} = 200 \mu\text{F}$$



$$= \frac{0.8}{(20 \times 10^{-3}) \times 8 \times (25000)} = 200 \mu\text{F} \Rightarrow \boxed{C = 200 \mu\text{F}}$$

SWITCHING MODE POWER SUPPLY


- * AC to DC converter
- * used in CPU

$$f = \frac{1}{2\pi\sqrt{LC}}$$

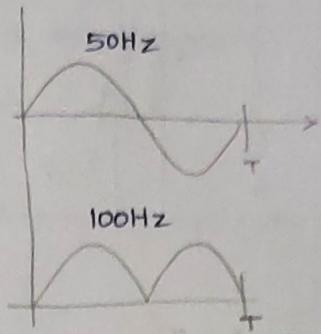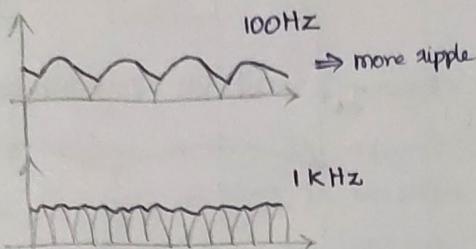
- * If frequency is high, less values of L and C is needed to filter out the pulsating dc.



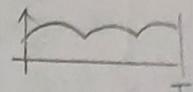3-φ semi-converter is a 3 pulse converter $f = 150\text{Hz}$



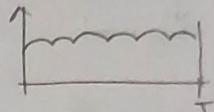3-φ full converter is 6-pulse converter $f = 300\text{Hz}$



- * Large inductance will require large size inductors
- * In laptops we can't have large size inductors (transformers) for converting AC to DC.

^{SiC}
* Silicon Carbide & Gallium Nitride (GaN) are now used instead of silicon wafer \Rightarrow ~~Si~~ t_{rr}



$$\text{SiC} \Rightarrow t_{rr} = 1 \text{ nano second}$$

$$\text{GaN} \Rightarrow t_{rr} = 10 \text{ pico second}$$


\Rightarrow So SiC and GaN can be used in fast switching devices.

\Rightarrow Flyback, Forward, Push-pull, Half bridge, Full-bridge \Rightarrow types of SMPS


FLYBACK SMPS

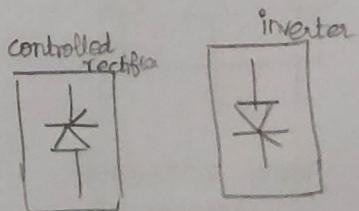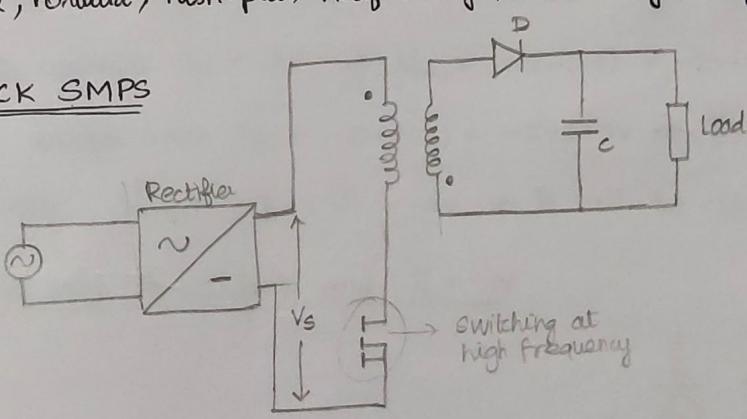

During Ton

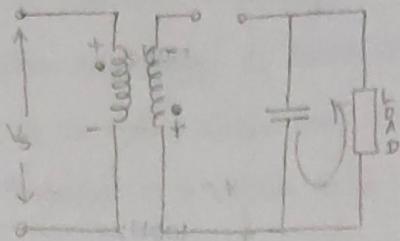


During Toff

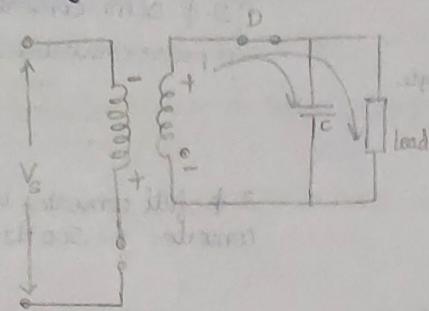

saturation of CA & DC


475 miliampere

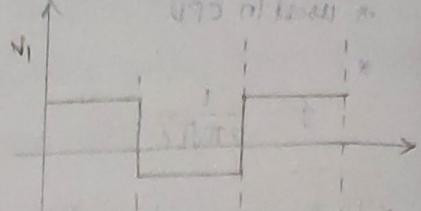

for saturation the field is to increase by 1/2

if there is 2 turns then

it's preheating

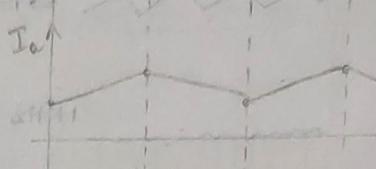

agent current like waveform agent
induction coil

saturation of forward winding and reverse field winding are equal at
DC at 5A

$$V_1 \quad V_2$$

$$\text{forward } V_{\text{total}} = V_1 + V_2$$

~~so $V_1 + V_2 = 0 \Rightarrow V_1 = -V_2$ first winding is direct polarity
and 2nd \leftarrow reverse polarity~~

(mt)

Forward:

because in 1st 3 windings are magnetically
coupling

so $V_1 = V_2$

Tertiary winding is for reset.

so when primary temp. is low so no heat loss so 3C or 4


so we do except right i.e. left, right, left, right, forward, forward

LIAZYOK 3WB

THREE PHASE CONVERTER

3φ full converter

3φ semi converter

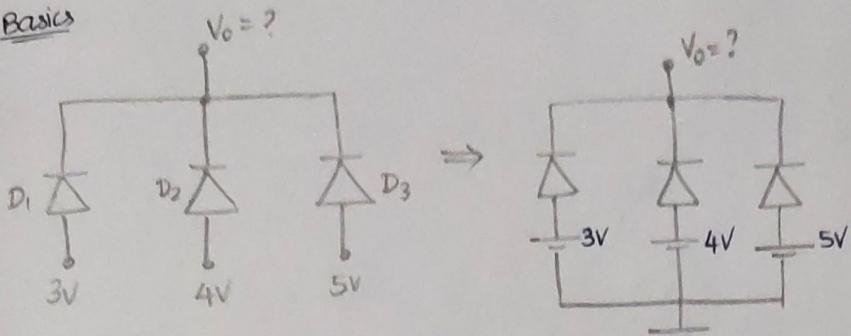Basics

The anode voltages of diodes are different, hence these diodes are not connected in parallel.

* Assume first 3V diode D_1 starts conducting, then $V_o \leq 3V$



* Now voltage across $D_2 = (4-3)V \Rightarrow$ So D_2 will start to conduct

* Now $V_o \leq 4V \Rightarrow$ Now D_1 becomes rev. biased.

* Voltage across $D_3 = V_{AK_3} = (5-4)V \Rightarrow D_3$ starts conducting. $\Rightarrow D_2$ rev bias

Hence $V_o = 5V$ This is the final value of V_o .

Only diode D_3 will conduct.

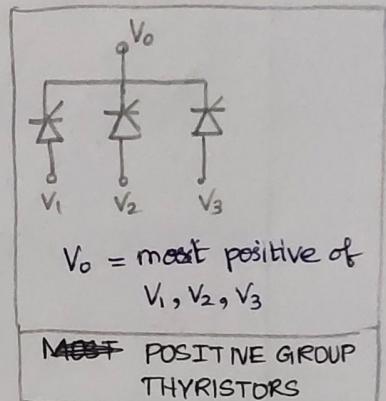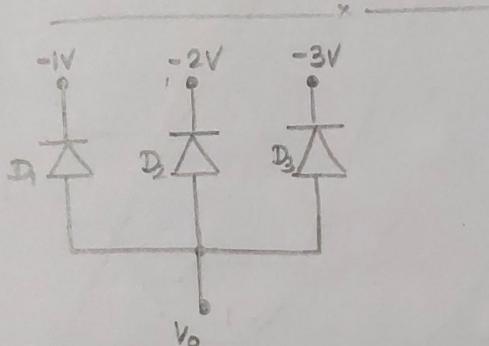

* Assuming initially D_1 conducts, $V_o = -1V \Rightarrow$ Voltage across D_2


$$\text{is } V_{AK_2} = -1 - (-2) = -1 + 2 = 1V \Rightarrow D_2 \text{ starts conducting.}$$

* As D_2 conducts $V_o = -2V \Rightarrow V_{AK_1} = -2 - (-1) = -2 + 1 = -1V \Rightarrow D_1$ off

* Now voltage across $D_3 = -2 - (-3) = -2 + 3 = 1V \Rightarrow D_3$ starts conducting

* $V_o = -3V \quad V_{AK_3} = -3 - (-2) = -1V \Rightarrow D_2$ will be off

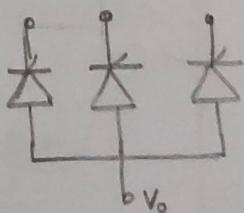
Finally only D_3 conducts and $V_o = -3V$



NEGATIVE GROUP THYRISTORS

$V_o = \text{most negative i/p}$


Assuming $\alpha=0^\circ$ (firing angle)

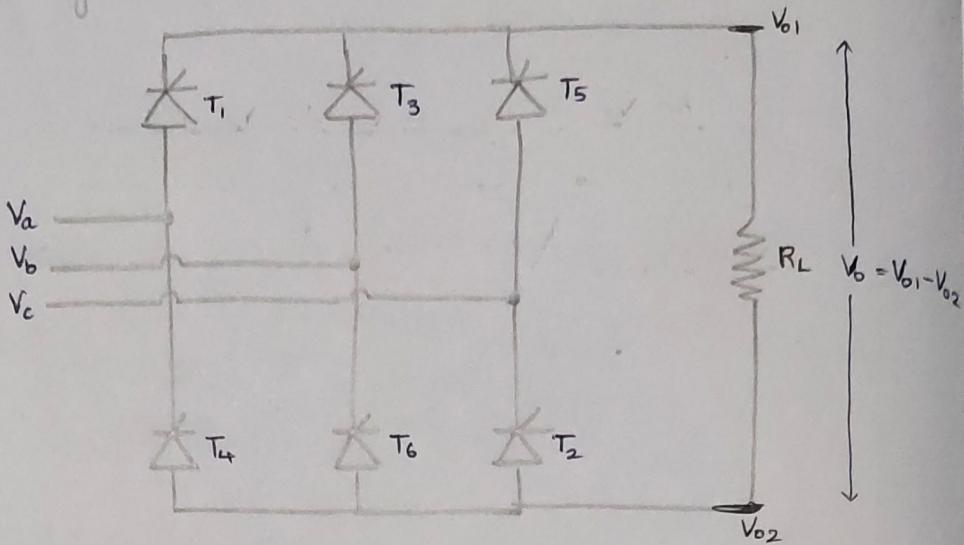

Hence $V_o = (\text{most positive}) - (\text{most negative})$

* At any time, o/p voltage is line voltage
(voltage between any two live lines)

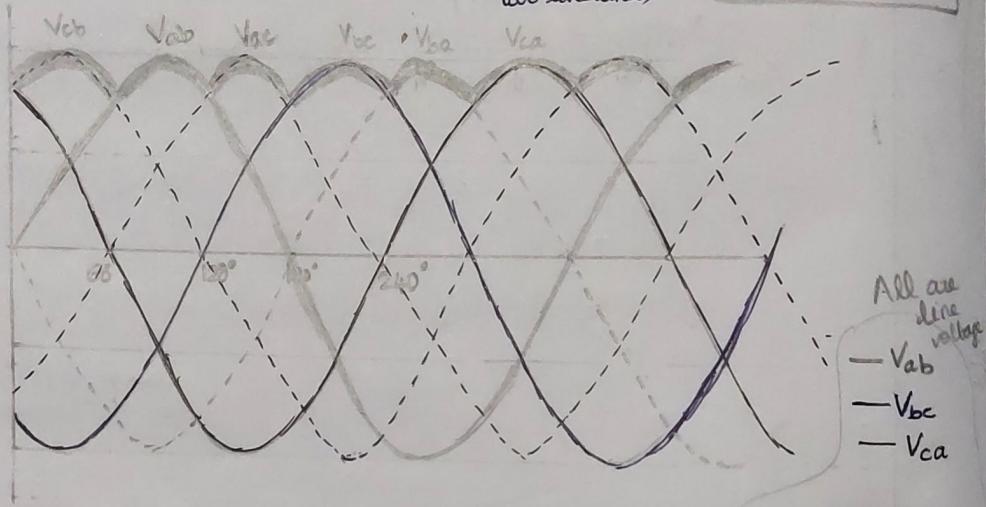Thyristor with
firing angle $\alpha=0^\circ$
is a diode



* V_{ab} starts at 0° ; V_{bc} starts at 120° ; V_{ca} starts at 240°

$$\begin{aligned} \dots &\rightarrow -V_{ab} = V_{ba} \\ \dots &\rightarrow V_{cb} \\ \dots &\rightarrow V_{ac} \end{aligned}$$

Consider 0° to 60° ,


$V_o = \text{most positive line voltage} =$

$$\begin{aligned} V_o &= \text{most positive} - (\text{most negative}) \\ &= \text{most positive} - \text{most negative} \end{aligned}$$

So from 0° to 60° , o/p voltage = V_{cb}

o/p voltage of 3- δ full converter

$\boxed{\alpha=0^\circ}$

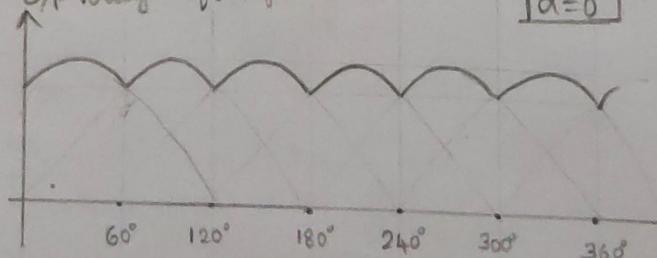

(1) For O/P = V_{cb} , T_5 is the +ve group thyristor that conducts (0° to 60°) T_6 is the -ve group thyristor that conducts.

	0° V_{cb}	60° V_{ab}	120° V_{ac}	180° V_{bc}	240° V_{ba}	300° V_{ca}	360°
$\alpha=0^\circ$	T_5	T_1	T_1	T_3	T_3	T_5	
	T_6	T_6	T_2	T_2	T_4	T_4	

Conduction table diagram

⇒ Each thyristor should conduct for 120° .

Initially, only one thyristor should be conducting (say T_1)

T_1 conducts ⇒ After 60° T_2 conducts ⇒ After 60° T_3 conducts, ...

When firing angle is $\alpha=60^\circ$,

	0°	60°	120°	180°	240°	300°	360°
	T_5	T_5	T_1	T_1	T_3	T_3	
	T_4	T_6	T_6	T_2	T_2	T_4	

V_{ca} V_{cb} V_{ab} V_{ac} V_{bc} V_{ba}

Sept 30 For a 3- ϕ full converter

$$V_o \text{ avg} = \frac{3V_{ml}}{\pi} \cos \alpha$$


$V_{ml} \Rightarrow$ maximum of line to line voltage

3- ϕ 440 V

line to line RMS voltage

$$\Rightarrow V_{ml} = 440\sqrt{2}$$

3- ϕ semi converter

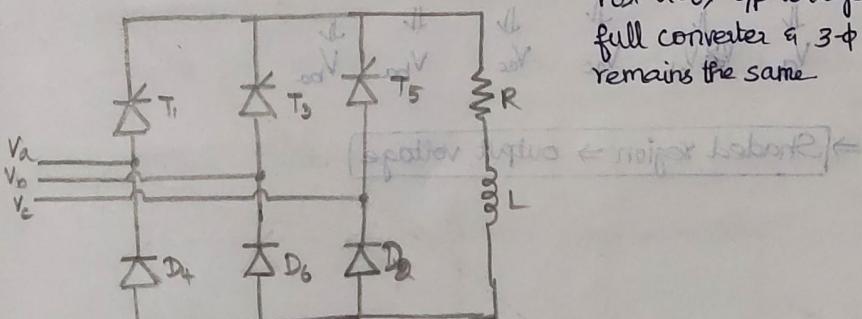


For $\alpha=0^\circ$, o/p voltage of 3- ϕ full converter & 3- ϕ semi-converter remains the same

	0° V_{cb}	60° V_{ab}	120° V_{ac}	180° V_{bc}	240° V_{ba}	300° V_{ca}	360°
$\alpha=0^\circ$	T_5	T_5	T_1	T_1	T_3	T_3	T_5
	D_6	D_6	D_2	D_2	D_4	D_4	


	0°	60°	120°	180°	240°	300°	360°
$\alpha=60^\circ$	T_5	T_5	T_1	T_1	T_3	T_3	
	D_6	D_6	D_2	D_2	D_4	D_4	

Thyristors are shifted by 60°

Diodes remain same

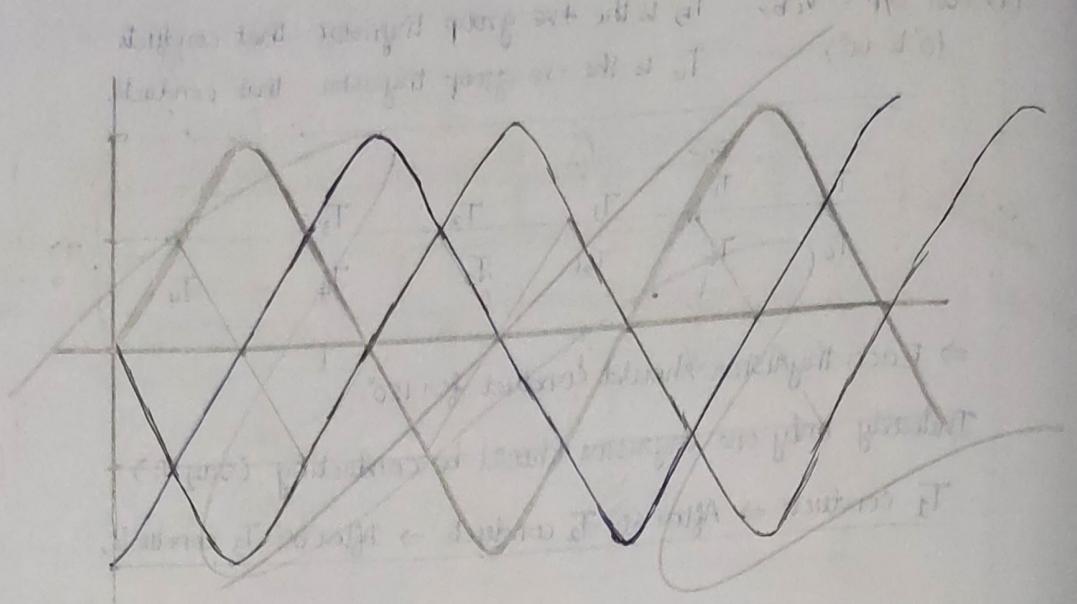



For $\alpha = 60^\circ$, semi-converter

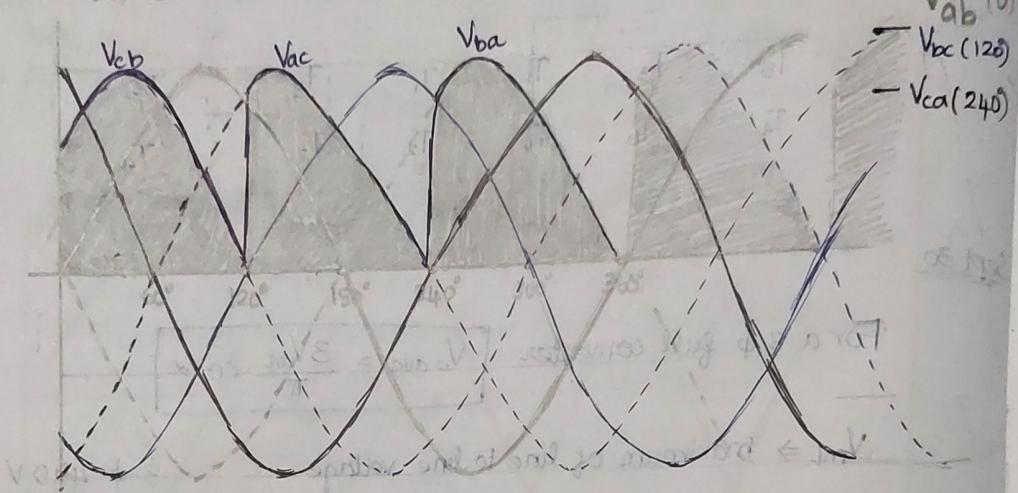


	0°	120°	180°	240°	300°	360°
T ₅	T ₅	T ₁	T ₁	T ₃	T ₃	
D ₆	D ₆	P ₂	D ₂	D ₄	D ₄	
V _{cb}	V _{cb}	V _{ac}	V _{ac}	V _{ba}	V _{ba}	

\Rightarrow Shaded region \Rightarrow output voltage

Line Commutated Inverter

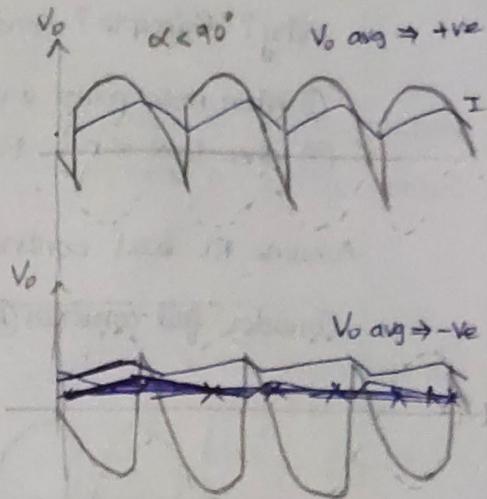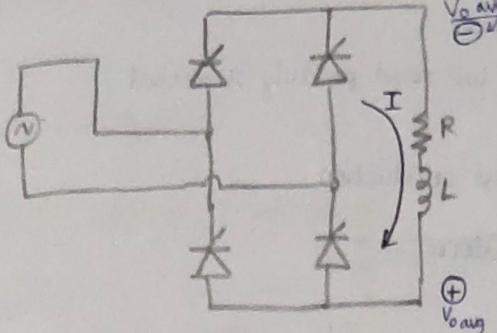

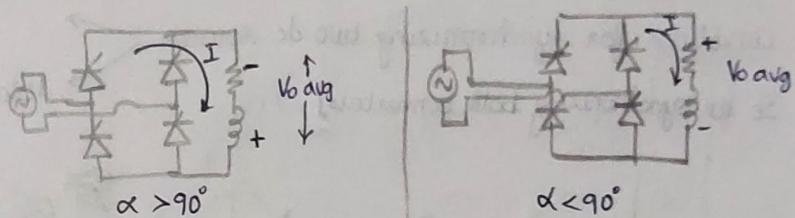- * When $\alpha > 90^\circ$, the $V_o \text{ avg}$ becomes negative \Rightarrow voltage polarity reverses.
- * But current direction remains same.



Current enters through -ve terminal
Current leaves through +ve terminal

The load acts as a DC source

Current enters through +ve terminal.

Load is acting as a load

DC \rightarrow AC \Rightarrow Inverter

Hence it is called line commutated inverter device and no commutation device is required.

If a rectifier is operated as an inverter, then ac line voltage commutes the device and no commutation device is required.



Line commutated inverter:

\Rightarrow 1φ full converter with RL load with continuous conduction & $\alpha > 90^\circ$

Q.4

Dual Converters (Back to back converters)

Similar to

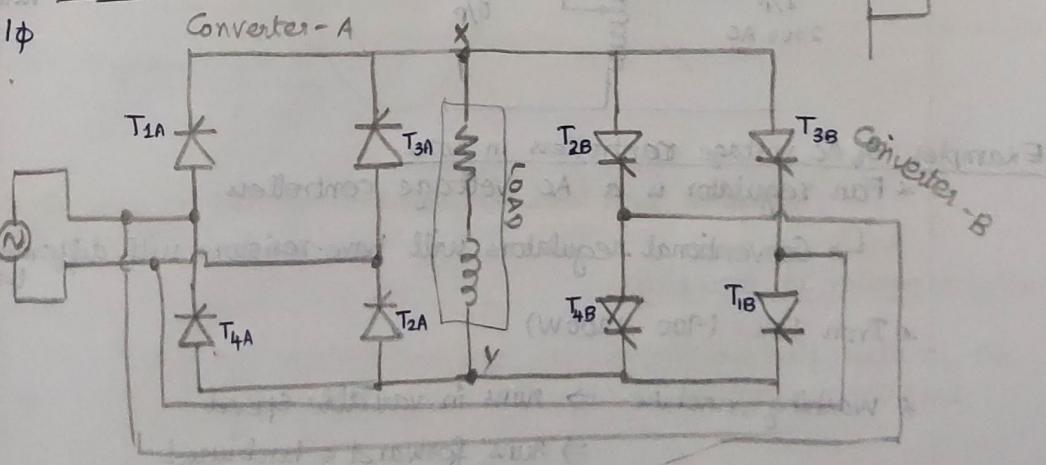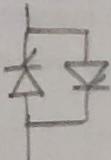


Why? Principle? Conditions?

- ① When more power is needed.
- ② When load is not RL , we need polarity reversal

Assume RL load, continuous conduction

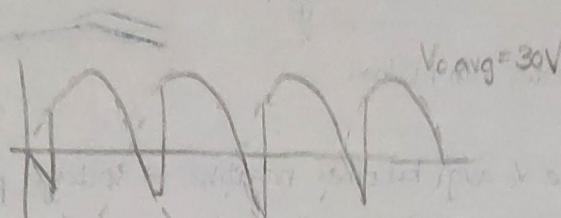Consider full converter A alone, $\alpha = 30^\circ$




Conditions for synchronizing two dc sources

So for synchronizing both converters,


Magnitude must be equal

Polarity must be

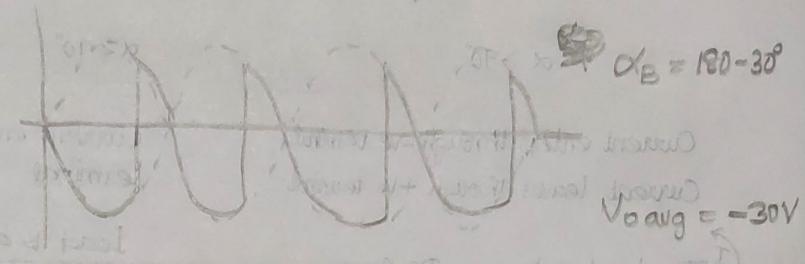


October
25

AC Voltage Controllers

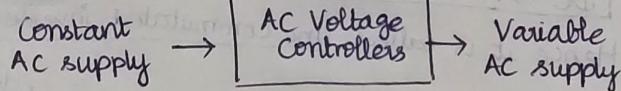

Example:- Variac

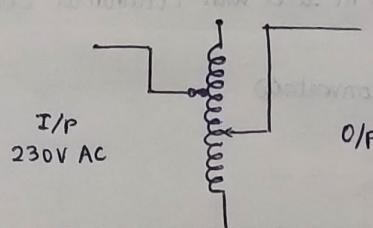

230V \rightarrow Variac \rightarrow (2-270)V
AC Variable

Examples of AC voltage controllers in home

* Fan regulator is an AC voltage controller.

\hookrightarrow Conventional regulators will have resistors with different tapping

* Iron box (900 - 1200W)

* Washing machine \Rightarrow runs in variable speed
 \Rightarrow runs forward & backward

Control Types


- (a) Phase control
- (b) Integral cycle control

Types


- (1) Half-Wave AC voltage control
- (2) Full-Wave AC voltage control

Basic AC voltage Controllers


Full Wave

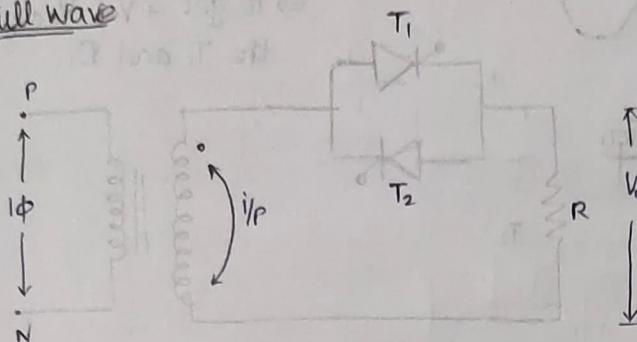

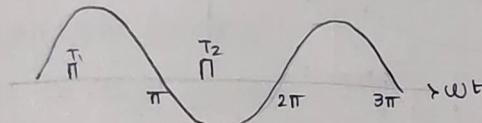* Two thyristors are needed or one triac  is needed to control two half cycles of AC voltage



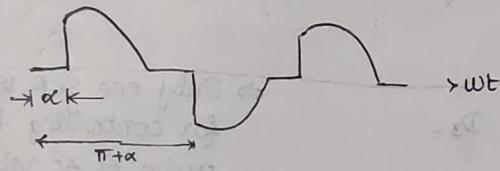V_o^2 will be the same as V_o^2 of 1φ full converter with R load.




$$\Rightarrow V_{o \text{ rms}} = \frac{V_m}{\sqrt{2\pi}} \sqrt{\pi - \alpha + \sin \frac{2\alpha}{2}}$$

$$\Rightarrow V_{o \text{ avg}} = 0V$$

Full Wave with RL load


V_A

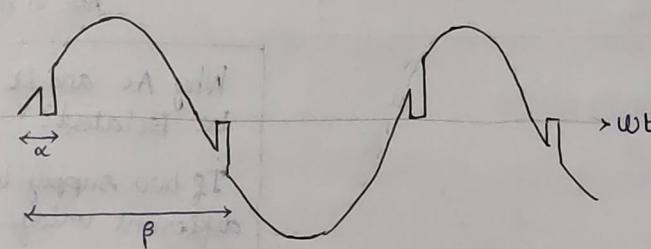

Types based on connections

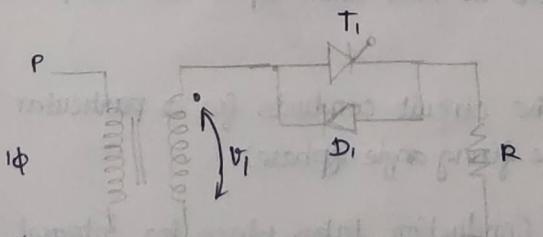
- (a) Series connection
- (b) Bridge connection

Half-Wave AC voltage controller (R load and RL load)



Half-wave AC voltage controller

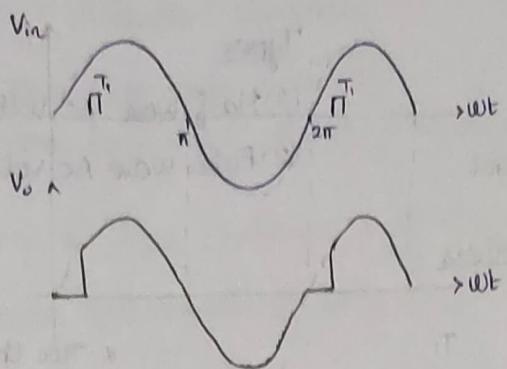
\Rightarrow Only one half cycle of the AC voltage is controlled.




$\Rightarrow V_o$ avg will be negative

\Rightarrow to get +ve V_o avg, interchange the T_i and D_i

(a) Series Connection

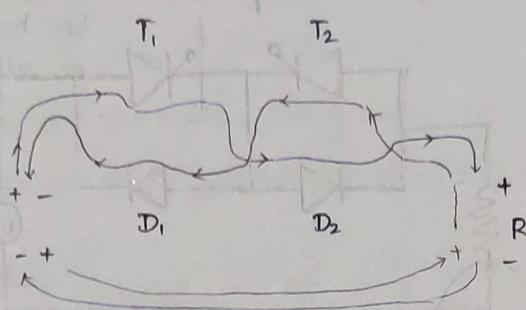

(b) Bridge Connection

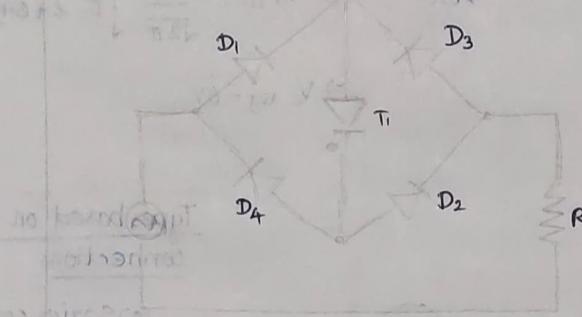

\Rightarrow Only one SCR is used for controlling both half cycles of AC Voltage

Ask in next class

Why AC and DC voltage should be isolated?



If two supply is with different voltage, we need isolation.

The AC voltage controllers we have seen up to now are phase control AC controllers.

In each half cycle, the circuit conducts for a particular part starting from some firing angle (α phase).

Integral Cycle Control: Conduction takes place for integral number of ~~full~~ full cycles and turn off for further number of cycles.

\rightarrow Used in systems with larger time constants.

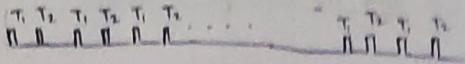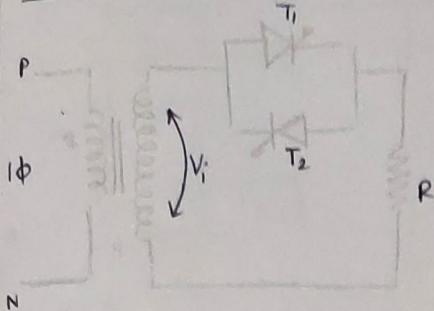October
26INTEGRAL CYCLE CONTROL

$$V_o \text{ rms} = \sqrt{\frac{\int_0^{6\pi} V_m^2 \sin^2 \omega t d(\omega t)}{10\pi}}$$

$$= \sqrt{\frac{6 \int_0^{\pi} V_m^2 \sin^2 \omega t d(\omega t)}{10\pi}}$$

$N \rightarrow \text{on cycles}$
 $M \rightarrow \text{no. of off cycles}$


$\Rightarrow 3$ cycles ON, 2 cycles OFF
Base is 10π

$$V_o \text{ rms} = \sqrt{\frac{N}{N+M} \int_0^{2\pi} V_m^2 \sin^2 \omega t d(\omega t)}$$

SEQUENTIAL CONTROL


There are many types of sequential control

(a) Two stage sequential control

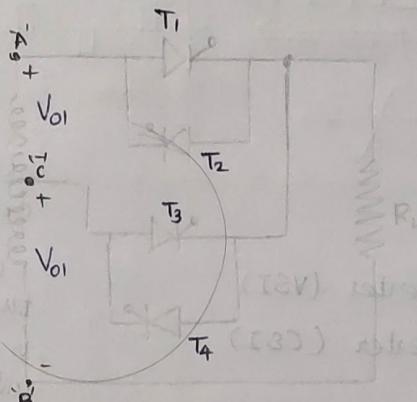


$$V_{AB} = 2V_{O1}; V_{AC} = V_{CB} = V_{O1}$$

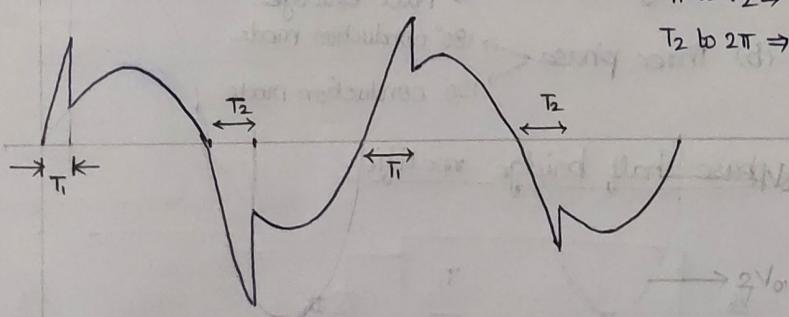0 to $T_1 \Rightarrow T_1$ thyristor on
 T_1 to $\pi \Rightarrow T_3$ thyristor on
 π to $T_2 \Rightarrow T_2$ thyristor on
 T_2 to $2\pi \Rightarrow T_4$ is on



We can get different wave shapes based on which thyristors we are firing.

3φ AC Voltage controllers

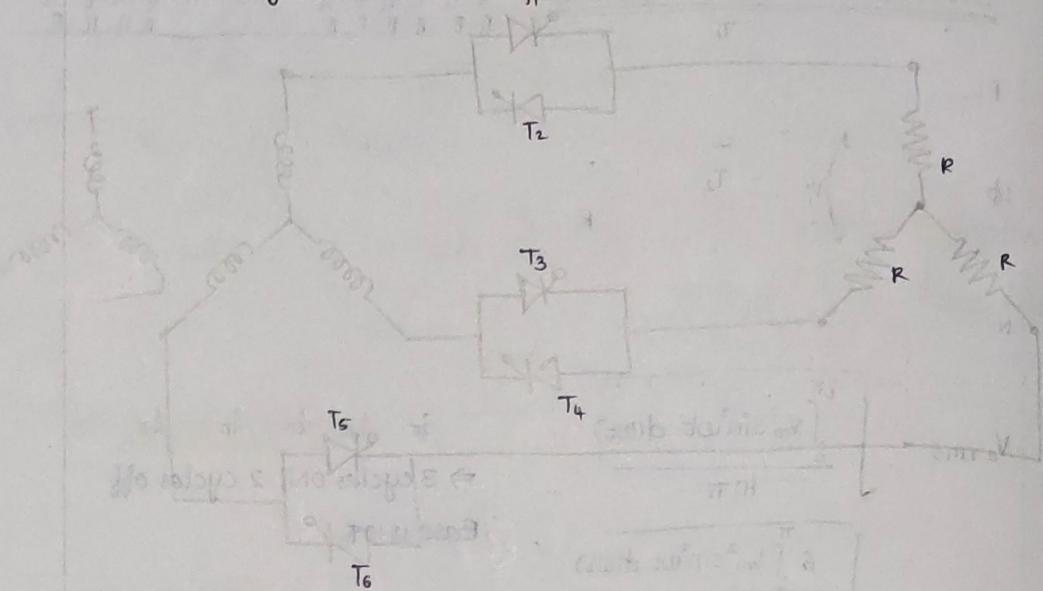


October 29


Inverter (DC to AC)

Types (Wave shapes)


(a) Square wave

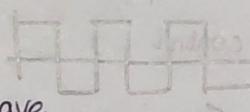

(b) Quasi square wave

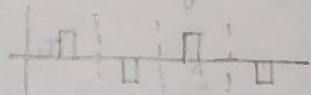

(c) Sine Wave

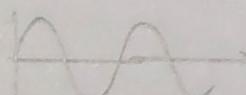

Types (source)

(a) Voltage source Inverter (VSI)

(b) Current source inverter (CSI)

UPS is needed for critical loads.


Computer will turn off even if there is a power cut for milli seconds,

UPS will turn ~~off~~ on immediately after power cut


Types (Phase)

- (a) Single phase
 - Half bridge
 - Full bridge
- (b) Three phase
 - 180° conduction mode
 - 120° conduction mode

Single phase half bridge rectifier

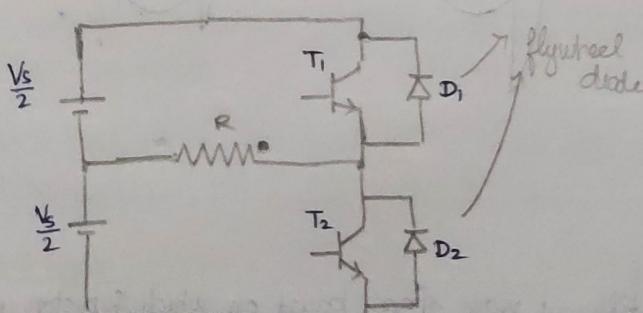


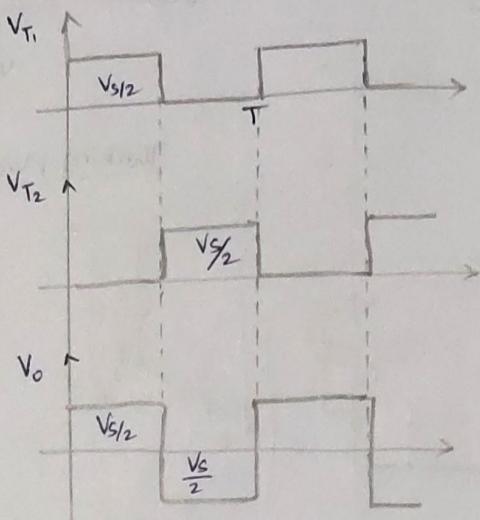If I want soft square wave
turn on T₁ for 10ms
and T₂ for 10 ms



1φ Full Bridge inverter (R-load)

for RL load

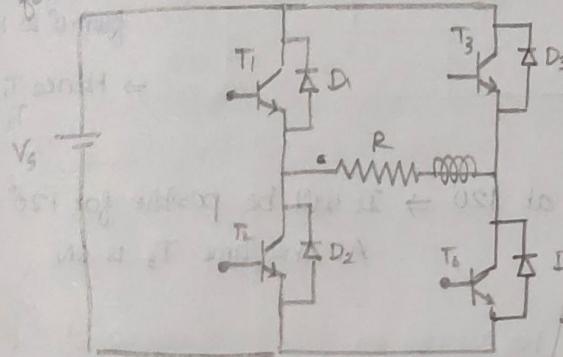

R load

Positive half cycle $\Rightarrow T_1$ and T_2 on

Negative half cycle $\Rightarrow T_3$ and T_4 on

RL load


\Rightarrow Initially T_1 & T_4 are on $\therefore V_{o1} = 0$.
Inductor charges $\frac{dV_o}{dt} = \frac{V_o}{L}$

$\Rightarrow T_1$ & T_4 are off


\Rightarrow Inductor polarity reverses $\frac{dV_o}{dt} = \frac{V_o}{L}$


\Rightarrow and starts discharging.

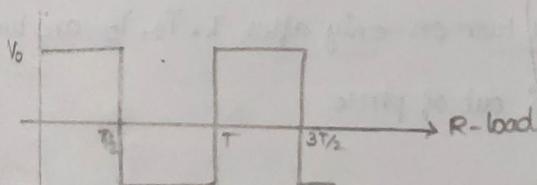\Rightarrow Due to inductor, T_3 and T_2 turn on




For RL load

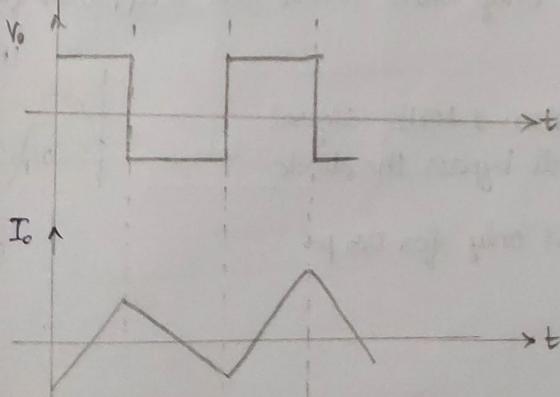

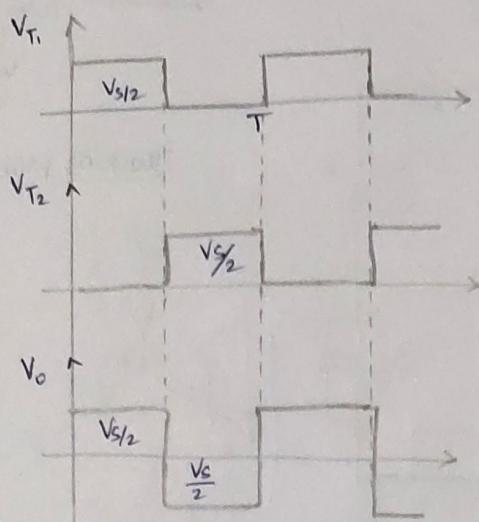

1φ Full Bridge inverter (R-load)

for RL load

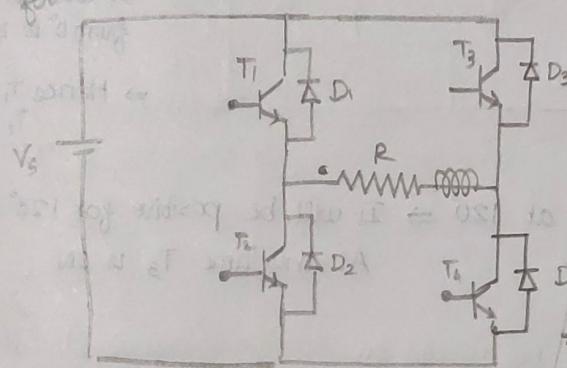

R load

Positive half cycle $\Rightarrow T_1$ and T_2 on

Negative half cycle $\Rightarrow T_3$ and T_4 on

RL load


\Rightarrow Initially T_1 & T_4 are on \Rightarrow voltage Inductor charges $\frac{500m}{+ -}$

$\Rightarrow T_1$ & T_4 are off


\Rightarrow Inductor polarity reverses $\frac{-500m}{- +}$

\Rightarrow and starts discharging.

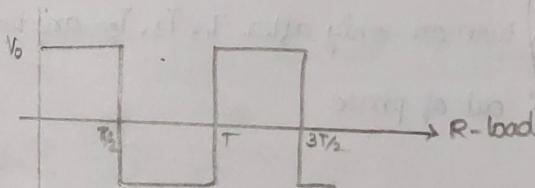
\Rightarrow Due to inductor, T_3 and T_2 turns on



For RL load

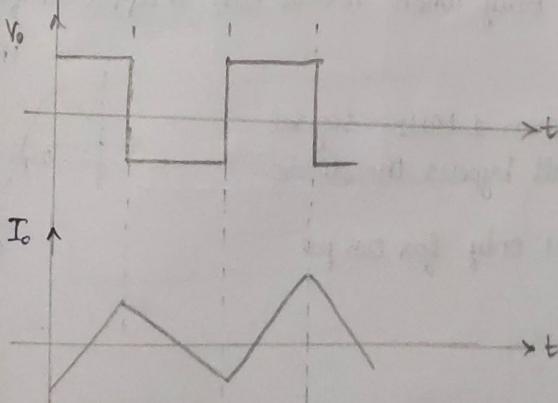

3^Φ Inverter 180° Conduction

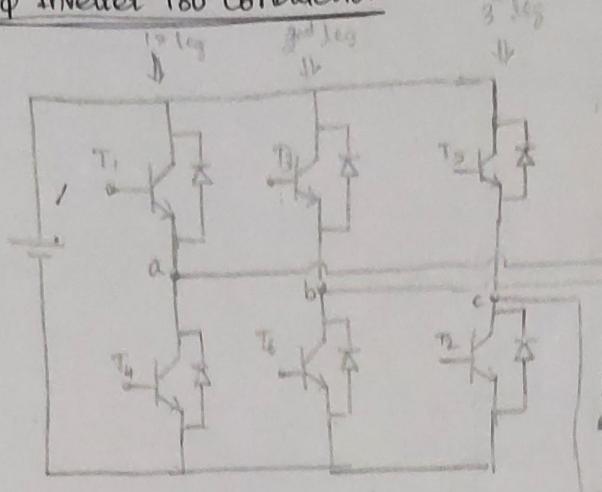

Inverter Vs UPS

↓
Very fast connection load.

Working principle same

	0°	30°	120°	180°	240°	300°	360°	
1 st leg \Rightarrow	T ₁			T ₄				Starts at 0°
2 nd leg \Rightarrow		T ₆		T ₃		T ₆		It will be positive from 0° to 180°
3 rd leg \Rightarrow	T ₅		T ₂		T ₅			Starts at 240° \Rightarrow Hence T ₁ conducts T ₂ is off

b phase will start at 120° \Rightarrow It will be positive for 120° to 300°
At this time T₃ is ON

Nov-8

T₁ and T₄ should not be turned on simultaneously \Rightarrow Short ckt

T₃ and T₆

T₅ and T₂

\Rightarrow T₄, T₆, T₂ should turn on only after T₁, T₃, T₅ are turned off

\Rightarrow T₄ & T₁ are 180° out of phase

T₃ & T₆

T₅ & T₂


10⁻⁶

1MHz

A diode will turn off only when reverse bias is applied for more than its t_{rr}

1MHz

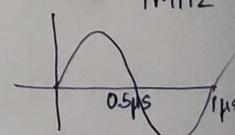
If t_{rr} = 1 μs \Rightarrow When 1 MHz signal will bypass the diode.



\Rightarrow Rev. bias is applied only for 0.5 μs

0.5μs


For 0° to 60° , T_1, T_4

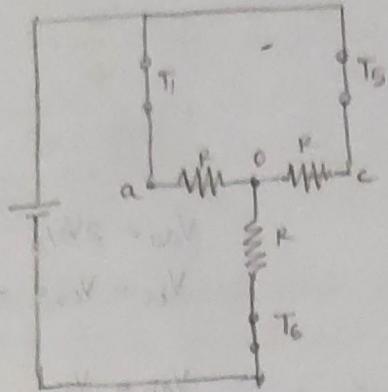

$$V_{ab} = V_{ca} = \frac{V_s}{3}$$

$$V_{bo} = -\frac{2V_s}{3}$$

(Polarity is negative)

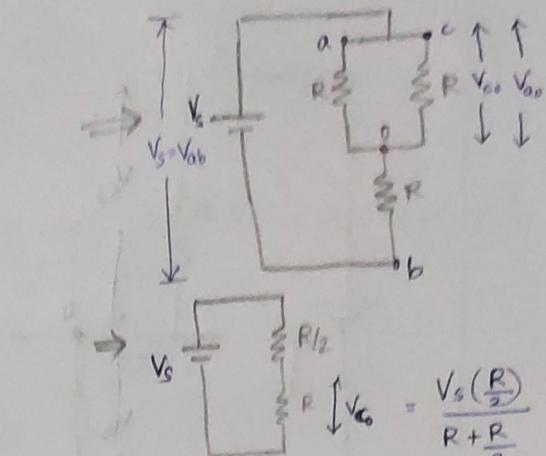


$$V_{bo} = -\frac{V_s(R)}{R+\frac{R}{2}} = \frac{V_s R}{2(2R+\frac{R}{2})}$$

$$= -\frac{V_s(2)}{(3)}$$


$$V_{co} = \frac{V_s}{3}$$

For 0° to 60°
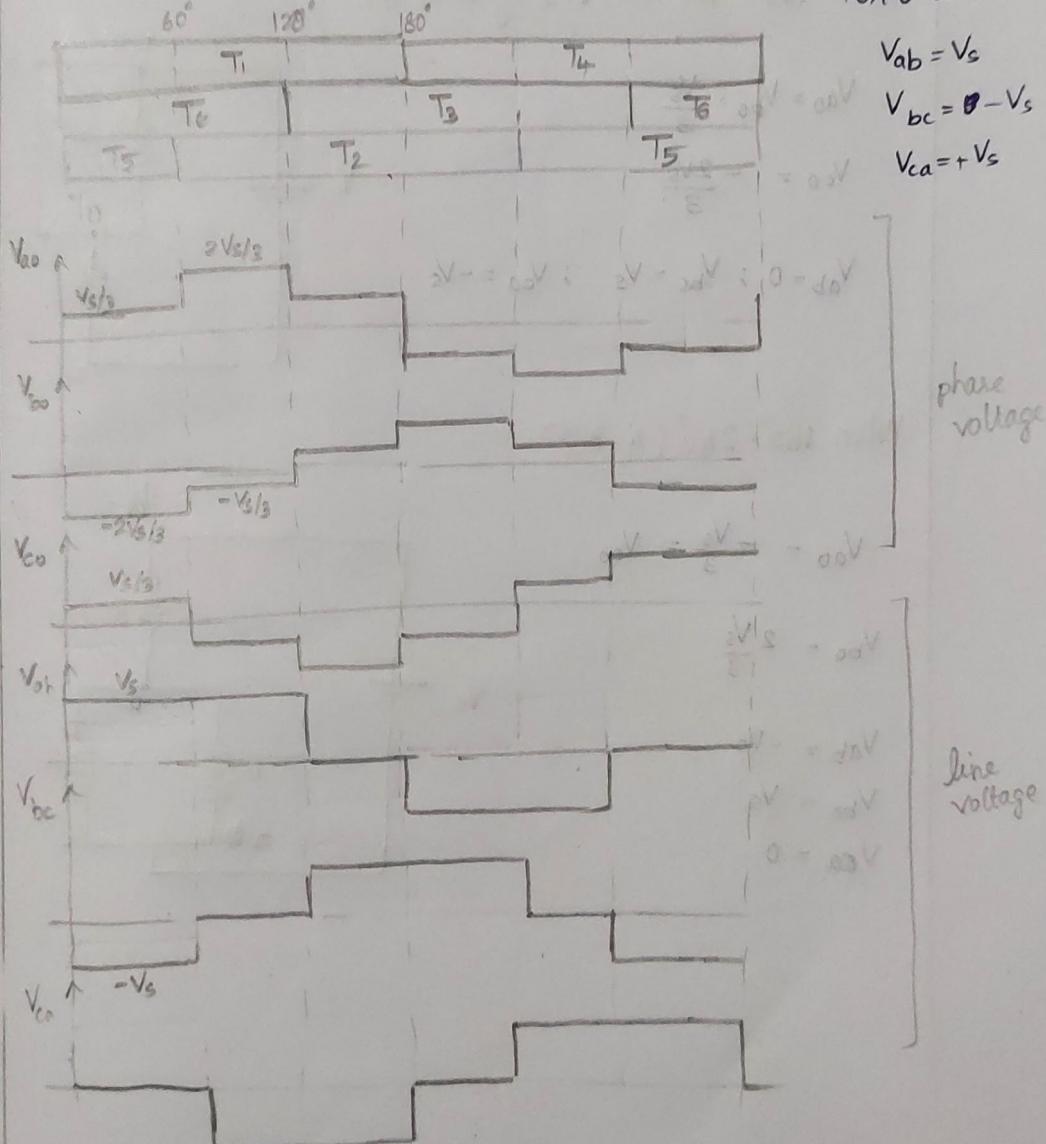
$$\begin{aligned} V_{ab} &= V_s \\ V_{bc} &= 0 - V_s \\ V_{ca} &= +V_s \end{aligned}$$



When 60° to 120°
 T_1, T_2, T_3

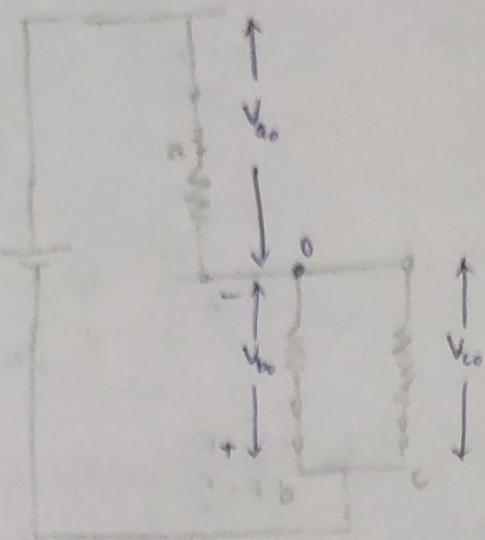

$$V_{a0} = \frac{2Vs}{3}$$

$$V_{bo} = V_{co} = -\frac{Vs}{3}$$

$$V_{ab} = Vs$$

$$V_{bc} = 0$$


$$V_{ca} = -Vs$$

When 120° to 180° (3, 2, 3 Tappings on)

$$V_{a0} = V_{bo} = \frac{Vs}{3}$$

$$V_{co} = -\frac{2Vs}{3}$$
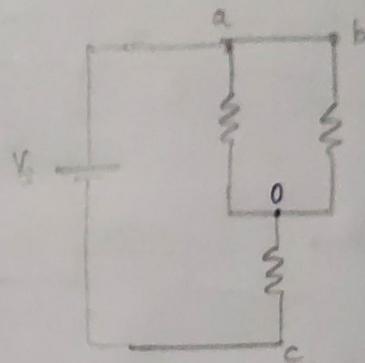
$$V_{ab} = 0 ; V_{bc} = Vs ; V_{ca} = -Vs$$



When 180° to 240° (4, 3, 2)


$$V_{a0} = -\frac{Vs}{3} = V_{co}$$

$$V_{bo} = 2\frac{Vs}{3}$$


$$V_{ab} = -Vs$$

$$V_{bc} = Vs$$

$$V_{ca} = 0$$

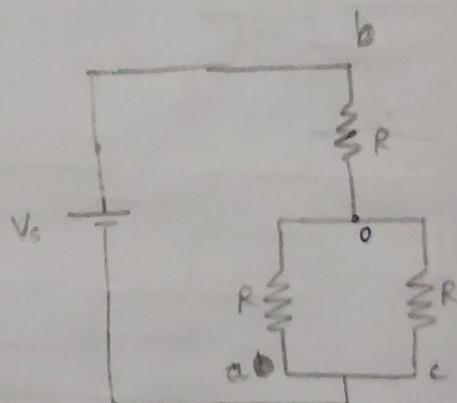

120° conduction mode

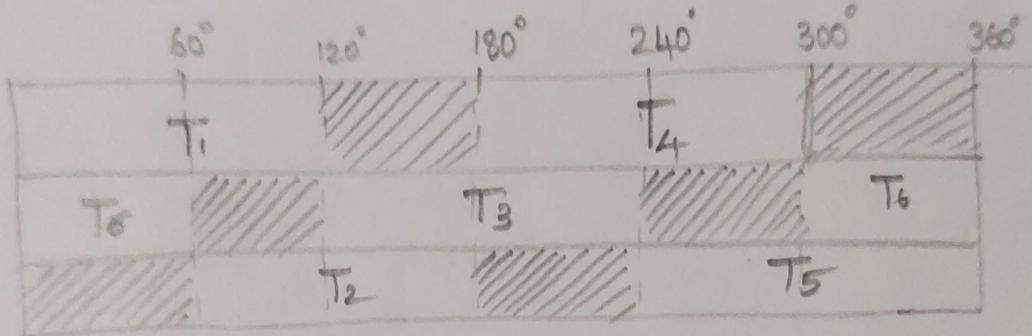

Same as 180° conduction mode but here first 120° degree it conducts, next 60° it will be off (shaded region)